

Dan Ports
6,002 B10

8/20 ~~28~~

1. A. $i_L = i_C + i_L = -C \frac{dv_C}{dt} + i_L = -LC \frac{d^2 i_L}{dt^2} + i_L$

$$\frac{d^2 i_L}{dt^2} + \frac{i_L}{LC} = \frac{I_S}{LC} \Rightarrow s^2 + \frac{1}{LC} = 0 \Rightarrow s = \pm \frac{j}{\sqrt{LC}}$$

$$i_L = I_S$$

$$i_{LH} = A \cos\left(\frac{1}{\sqrt{LC}} t\right) + B \sin\left(\frac{1}{\sqrt{LC}} t\right)$$

$$i_L(0) = I_S + A = 0 \Rightarrow A = -I_S$$

$$v_C(0) = L \frac{di_L}{dt}\bigg|_0 = B = 0 \Rightarrow B = 0$$

$$i_L(t) = I_S - I_S \cos\left(\frac{1}{\sqrt{LC}} t\right) \quad \text{for } t > 0$$

b. $i_{Lp} = 0$

$$i_{LH} = A \cos\left(\frac{1}{\sqrt{LC}} t\right) + B \sin\left(\frac{1}{\sqrt{LC}} t\right)$$

$$i_L(0) = A = I_L \Rightarrow A = I_L$$

$$v_C(0) = L \frac{di_L}{dt}\bigg|_0 = B = 0 \Rightarrow B = 0$$

$$i_L(t) = I_L \cos\left(\frac{1}{\sqrt{LC}} t\right)$$

c. $i_{Lp} = I_S$

$$i_{LH} = A \cos\left(\frac{1}{\sqrt{LC}} t\right) + B \sin\left(\frac{1}{\sqrt{LC}} t\right)$$

$$i_L(0) = I_S + A = I_L \Rightarrow A = I_L - I_S$$

$$v_C(0) = L \frac{di_L}{dt}\bigg|_0 = B = 0 \Rightarrow B = 0$$

$$i_L(t) = I_S + (I_L - I_S) \cos\left(\frac{1}{\sqrt{LC}} t\right)$$


$$2. \quad v_o(t) = v_s(t) - v_c(t) \Rightarrow v_c(t) = v_s(t) - v_o(t)$$

$$C \frac{dv_c(t)}{dt} + \frac{v_c(t)}{R_2} = \frac{v_s(t)}{R_2}$$

$$\Rightarrow \frac{v_c(t)}{R_2} + C \frac{dv_c(t)}{dt} = \frac{v_s(t)}{R_2}$$

$$\Rightarrow \frac{v_s(t) - v_o(t)}{R_2} + C \frac{d(v_s(t) - v_o(t))}{dt} = \frac{v_o(t)}{R_2}$$
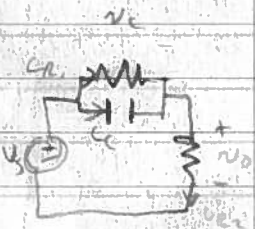
$$\Rightarrow \frac{v_s(t)}{R_2} + C \frac{dv_s(t)}{dt} - \frac{v_o(t)}{R_2} - C \frac{dv_o(t)}{dt} = \frac{v_o(t)}{R_2}$$



$$b) \quad \frac{v_s e^{j\omega t}}{R_1} + j\omega C v_s e^{j\omega t} = \frac{v_o e^{j\omega t}}{R_2} + j\omega C v_o e^{j\omega t}$$

$$\frac{v_s}{R_1} + j\omega C v_s = \frac{v_o}{R_2} + j\omega C v_o$$

$$v_s \left(\frac{1}{R_1} + j\omega C \right) = v_o \left(\frac{1}{R_2} + j\omega C \right)$$

$$\hat{v}_o = v_s \frac{\frac{1}{R_2} + j\omega C}{\frac{1}{R_1} + j\omega C} = v_s \frac{R_2 + R_1 R_2 j\omega C}{R_2 + R_1 + R_1 R_2 j\omega C}$$

$$v_o(t) = A \hat{v}_o e^{j\omega t} = v_s \frac{R_2 + R_1 R_2 j\omega C}{R_2 + R_1 + R_1 R_2 j\omega C} e^{j\omega t}$$

$$c) \quad v_s \text{ (constant)} = R_2 \left(\frac{v_s}{R_2} e^{j\omega t} \right)$$

$$\text{so } v_o(t) = R_2 \left(\frac{v_s}{R_2} e^{j\omega t} \right)$$

$$v_o(t) = v_s \frac{R_2 \sqrt{1 + R_1^2 \omega^2 C^2} e^{j(\omega t + \tan^{-1}(\omega C R_1))}}{\sqrt{R_2^2 + R_1^2 + 2 R_1 R_2 \omega^2 C^2} e^{j(\tan^{-1}(\frac{R_1 R_2 \omega C}{R_2 + R_1}))}}$$

$$= \frac{v_s \sqrt{1 + R_1^2 \omega^2 C^2}}{\sqrt{(R_2 + R_1)^2 + R_1^2 R_2^2 \omega^2 C^2}} e^{j(\omega t + \tan^{-1}(\omega C R_1) - \tan^{-1}(\frac{R_1 R_2 \omega C}{R_2 + R_1}))}$$

$$v_o(t) = R_2 \left(\frac{v_s}{R_2} e^{j\omega t} \right)$$


$$v_o(t) = \frac{R_2 v_s \sqrt{1 + R_1^2 \omega^2 C^2}}{\sqrt{(R_2 + R_1)^2 + R_1^2 R_2^2 \omega^2 C^2}} \cos(\omega t + \phi)$$

$$\text{Where } \phi = \tan^{-1}(\omega C R_1) - \tan^{-1}\left(\frac{R_1 R_2 \omega C}{R_2 + R_1}\right)$$

$$I_1 = \frac{V}{R + \frac{1}{j\omega C}} = \frac{V}{R + \frac{1}{j\omega C}} \quad \text{by parallel con}$$

$$V_1 = \frac{I_1 \cdot \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{I_1}{j\omega C R + 1} \quad \text{by series/parallel combination}$$
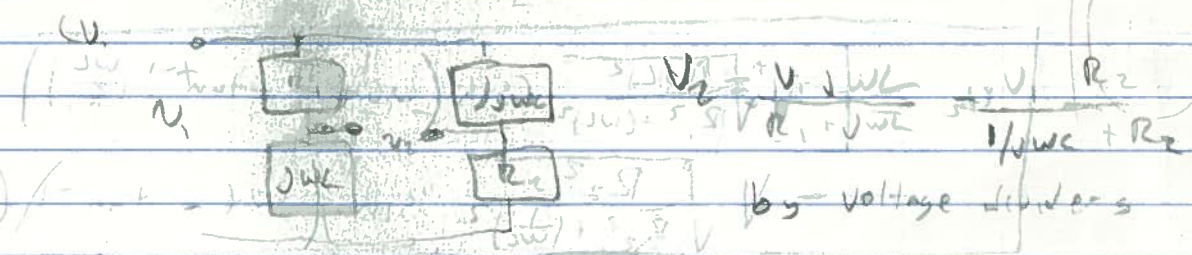
$$\frac{I_2}{I_1} = \frac{j\omega L + R_2}{j\omega L + R + \frac{1}{j\omega C}} \quad \text{by current divider rule}$$



$$H = \frac{V_2}{V_1} = \frac{j\omega L + R_2}{R_1 + j\omega L + \frac{1}{j\omega C} + R_2}$$

B. $V_1(t) = I_{rms} \cos(\omega t) = \text{Re}(I e^{j\omega t})$
 so $V_2(t) = \text{Re}(H(\omega) I e^{j\omega t})$

$$= \text{Re} \left[\frac{j\omega L + R_2}{j\omega L + R + \frac{1}{j\omega C} + R_2} I e^{j\omega t} \right]$$

$$= |H(\omega)| I \cos(\omega t + \phi) = \frac{I \sqrt{R_2^2 + (\omega L)^2}}{\sqrt{R^2 + (\omega L - 1/\omega C)^2}} \cos(\omega t + \phi)$$

$$\phi = \tan^{-1} \left(\frac{\omega L}{R_2} \right) - \tan^{-1} \left(\frac{\omega L - 1/\omega C}{R} \right)$$

e. $v_1(t) = V \sin(\omega t) = \text{Im}(V e^{j\omega t})$

So $v_2(t) = \text{Im}(H(j\omega) V e^{j\omega t})$

$$= \text{Im} \left[\frac{j\omega L}{R_1 + j\omega L} - \frac{R_2}{R_2 + 1/j\omega C} \right] V e^{j\omega t}$$

$$= \text{Im} \left[\frac{\sqrt{(\omega L)^2}}{\sqrt{R_1^2 + (\omega L)^2}} e^{j(\frac{\pi}{2} + \tan^{-1}(\frac{\omega L}{R_1}))} - \frac{\sqrt{R_2^2}}{\sqrt{R_2^2 + (\frac{1}{\omega C})^2}} e^{j(-\tan^{-1}(\frac{1/\omega C}{R_2}))} \right] \cdot (V e^{j\omega t})$$

(1)

$$v_2 = \frac{V}{\omega} \left[\frac{\omega L R_1}{\sqrt{R_1^2 + (\omega L)^2}} \sin\left(\omega t - \frac{\pi}{2} + \tan^{-1}\left(\frac{\omega L}{R_1}\right)\right) - \frac{R_2}{\sqrt{R_2^2 + (\frac{1}{\omega C})^2}} \sin\left(\omega t - \tan^{-1}\left(\frac{1}{\omega C R_2}\right)\right) \right]$$

$v_2(t) = 0$

9. a. $v_+ = v = 10 \text{ V} \sin(10^9 t)$

$$z_+ = \frac{-10 \text{ V}}{5 \text{ mA}} e^{-j\pi/6} = -2 \text{ k}\Omega e^{j\pi/6}$$

$$z_+ = -2 \text{ k}\Omega \left[\frac{\sqrt{3}}{2} + j \frac{1}{2} \right]$$

(2)

$$i = \frac{-10 \text{ V} e^{j\omega t}}{z_+} = \frac{-10 \text{ V} e^{j\omega t}}{-\sqrt{3} \text{ k}\Omega + j \frac{1}{2} \text{ k}\Omega + 2j \text{ k}\Omega} = \frac{-10 \text{ V}}{-\sqrt{3} - \sqrt{3}j/2} e^{j\omega t}$$

$$= \frac{10}{\sqrt{3}} \left(\frac{1}{1 + j\sqrt{3}} \right) e^{j\omega t} = \frac{10}{\sqrt{3}} \cdot \frac{1}{2} e^{-\arctan \sqrt{3}} e^{j\omega t}$$

$$= \frac{5}{\sqrt{3}} e^{j\omega t - \pi/3}$$

$$i(t) = \text{Im}(i) = \frac{5}{\sqrt{3}} \sin(10^9 t - \pi/3) \text{ mA}$$

5. a. $P = I^2 R = \left(\frac{V_s}{R_s + R_L} \right)^2 \cdot R_L = \frac{V_s^2 R_L}{(R_s + R_L)^2}$

$\frac{dP}{dR_L} = \frac{-(R_L - R_s) V_s^2}{(R_s + R_L)^3}$. This equals 0 when $R_s = R_L$.

So P is maximized at $R_s = R_L$.

At $R_s = R_L$, $P = \frac{V_s^2 R_L}{(R_L + R_L)^2} = \frac{V_s^2 R_L}{4R_L^2} = \frac{V_s^2}{4} R_L$

b. $\bar{P} = \frac{W}{2\pi} \int_0^{2\pi/W} R \left(\frac{1}{I} \cdot e^{j\omega t} \right)^2 dt = \frac{W}{2\pi} \int_0^{2\pi/W} |I|^2 \cos^2(\omega t) dt$
 $= \frac{W}{2\pi} R |I|^2 \int_0^{2\pi/W} \cos^2(\omega t) dt = \frac{WR |I|^2}{2\pi} \int_0^{2\pi/W} \frac{1 + \cos(2\omega t)}{2} dt$
 $= \frac{WR |I|^2}{2\pi} \left[t - \frac{\sin(2\omega t)}{2\omega} \right]_{t=0}^{t=2\pi/W}$
 $= \frac{WR |I|^2}{2\pi} \left[\frac{2\pi}{W} - (0 - 0) \right] = \frac{|I|^2 R}{2}$

c. $I = \frac{V_s}{Z_L + R_s} = \frac{V_s}{R_s + R_L + jX_L} \Rightarrow |I| = \frac{V_s}{\sqrt{(R_s + R_L)^2 + X_L^2}}$

$\bar{P} = |I|^2 R_L / 2 = \frac{V_s^2 R_L}{2(R_s + R_L)^2 + X_L^2}$

X_L must be zero to minimize the denominator and maximize the power. with $X_L = 0$,

$\bar{P} = \frac{V_s^2 R_L}{2(R_s + R_L)^2}$. From part a, we know

this is maximized when $R_s = R_L$

d. i. $Z = \frac{R_L / j\omega C}{R_L + 1/j\omega C} = \frac{R_L}{(R_L \omega C)^2 + 1} - \frac{j R_L^2 \omega C}{(R_L \omega C)^2 + 1}$

ii. $\frac{R_L}{(R_L \omega C)^2 + 1} = R_s \Rightarrow R_L = R_s ((R_L \omega C)^2 + 1)$

$\Rightarrow R_L - R_s = (R_L \omega C)^2 \Rightarrow \frac{R_L - R_s}{R_L^2 R_s} = (\omega C)^2$

$\Rightarrow \omega C = \frac{1}{R_L} \cdot \sqrt{\frac{R_L}{R_s} - 1}$

$$0 = j\omega L - \frac{1}{j\omega C} \frac{(R_L)^2 \omega C}{(R_L \omega C)^2 + 1}$$

$$\omega C = \frac{R_L^2 \cdot \frac{1}{R_L} \sqrt{\frac{R_L}{R_S - 1}}}{R_L^2 \cdot \frac{1}{R_L^2} (R_L/R_S - 1) + 1}$$

$$\omega C = \frac{R_L \sqrt{R_L/R_S - 1}}{R_L/R_S} = \boxed{R_S \sqrt{R_L/R_S - 1}}$$

For $R_L < R_S$, change the roles of the inductor and capacitor: let the inductor set the real part of the impedance to R_S and let the capacitor adjust the reactance to zero.

