


Dan Ports  
6.002 PS2

(2) As. i. This is a combination of series and parallel resistors.



$$R_T = \left( \frac{1}{R_1} + \frac{1}{R_2 + R_3} \right)^{-1} = \frac{R_1(R_2 + R_3)}{R_1 + R_2 + R_3}$$


ii. Consider  $V_s$  as a short circuit.

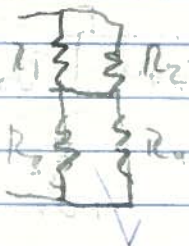

By combination of series/parallel circuits,


$$R_T = \frac{R_1 R_2}{R_1 + R_2} + \frac{R_3 R_4}{R_3 + R_4}$$

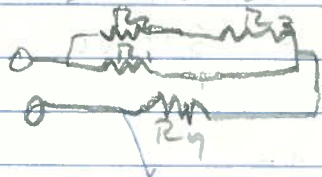iii. Consider  $I_s = 0 \Rightarrow$  open circuit. Then  $R_3$  is disconnected and can be ignored.





$$R_T = \frac{R_1(R_2 + R_3)}{R_1 + R_2 + R_3} + R_4$$

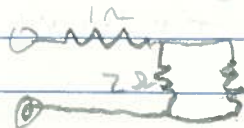iv. Combining the series resistors on the right side.



Thus  $R_T = 1R + \frac{3R \cdot 2R}{3R + 2R}$   
 $= 1R + \frac{6}{5}R = \frac{11}{5}R$

v. By series/parallel combinations

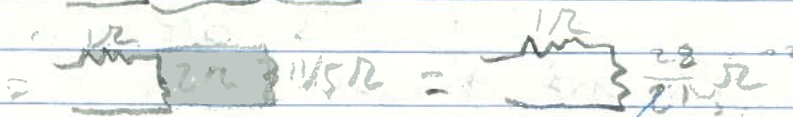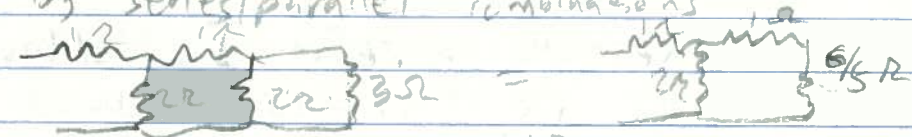

$$\frac{11}{5}R = R_{T4}$$

B.I.

$$R_{n+1} = \left( \frac{2R \cdot R_n}{2R + R_n} \right) + 1\Omega \quad \checkmark$$

$$\text{ii. } \lim_{n \rightarrow \infty} R_n = \lim_{n \rightarrow \infty} R_{n+1} = R_{\infty}$$

$$\text{Thus } R_{\infty} = \frac{2R R_{\infty}}{2R + R_{\infty}} + 1\Omega \quad \textcircled{1}$$

$$\Rightarrow 2R R_{\infty} + R_{\infty}^2 = 2R R_{\infty} + 2R^2 + 2R R_{\infty} - 1R$$

$$\Rightarrow R_{\infty}^2 - R_{\infty} + 1\Omega^2 - 2R^2 = 0$$

$$\Rightarrow R_{\infty} = 2R \text{ or } R_{\infty} = -1\Omega \text{ (extraneous)}$$

$$\boxed{R_{\infty} = 2R} \quad \checkmark$$

The answers from above are approaching  $R_{\infty}$

$$\textcircled{2} \text{ i. } \left[ R_{Th} = \frac{R_1 (R_2 + R_3)}{R_1 + R_2 + R_3} \right] \quad \checkmark \text{ from 2.1a(i)}$$

As the circuits are identical except for the voltage source. By the voltage divider relation,

$$V_{Th} = V_s \frac{R_2 + R_3}{R_1 + R_2 + R_3} \quad \checkmark$$

Short-circuiting the terminals gives

$$\boxed{I_{sc} = \frac{V_s}{R_1}} \quad \checkmark$$

$$\text{ii. From above } \left[ R_{Th} = \frac{R_1 (R_2 + R_3)}{R_1 + R_2 + R_3} \right] \quad \checkmark$$

The full current  $I_{sc}$  flows through  $R_1$  and returns through  $R_1$  with the terminals open, so the current through  $R_1$  and  $R_2$  must therefore be, by the current divider relation,

$$I_s \frac{R_3}{R_1 + R_2 + R_3}$$

Thus the voltage drop across  $R_1$

$$\text{is } I_s \frac{R_1 R_3}{R_1 + R_2 + R_3} \text{ and across } R_1$$



$\Delta V = I_S R_4$ , The open-circuit voltage across the terminals is the sum of these


$$V_{Th} = V_{oc} = I_S \frac{R_1 R_3}{R_1 + R_2 + R_3} + I_S R_4 \quad \checkmark$$

$$I_{N} = \frac{V_{Th}}{R_{Th}} = \frac{I_S \frac{R_1 R_3}{R_1 + R_2 + R_3} + I_S R_4}{\frac{R_1 (R_2 + R_3)}{R_1 + R_2 + R_3} + R_4} \quad \checkmark$$

$$I_N = \frac{I_S R_1 R_3 + I_S (R_1 + R_2 + R_3) R_4}{R_1 (R_2 + R_3) + (R_1 + R_2 + R_3) R_4}$$

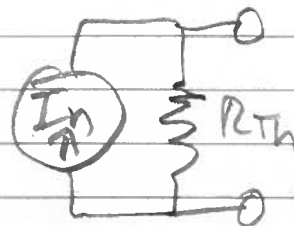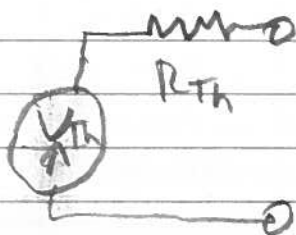These two circuits can be replaced with either of the following equivalent circuits, with their respective  $R_{Th}$ ,  $V_{Th}$ , and  $I_N$  values:




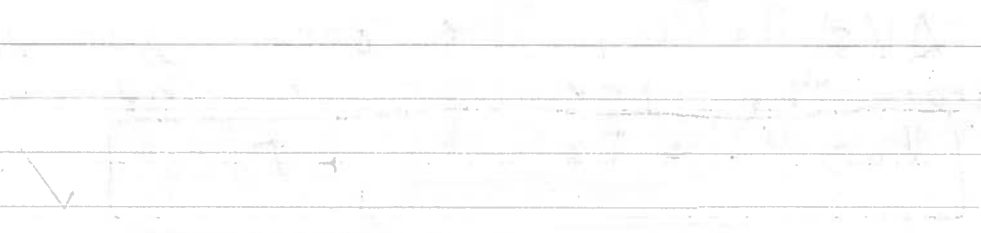


$\frac{1}{2} \rho v^2 C_d A$   
 $\frac{1}{2} \rho v^2 C_d A$   
 $\frac{1}{2} \rho v^2 C_d A$



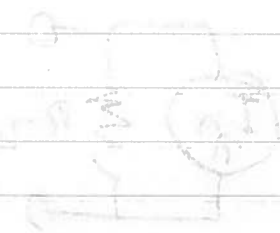
The force exerted by the wind on the sail is  
 given by the equation  
 $F = \frac{1}{2} \rho v^2 C_d A$




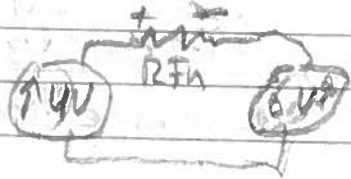
3a.  $V_{Th} = I \cdot R = 2\text{mA} \cdot 2\text{k}\Omega = 4\text{V}$  X



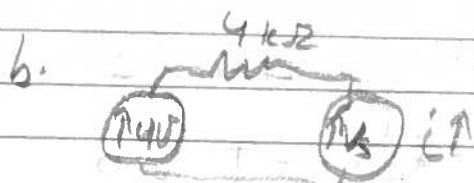This circuit implies that  
 $(4-6)\text{V} = iR$   
 $\Rightarrow -2\text{V} = -1\text{mA} R_{Th}$   
 $\Rightarrow R_{Th} = 4\text{k}\Omega$  X



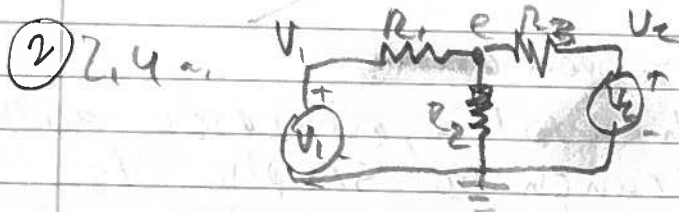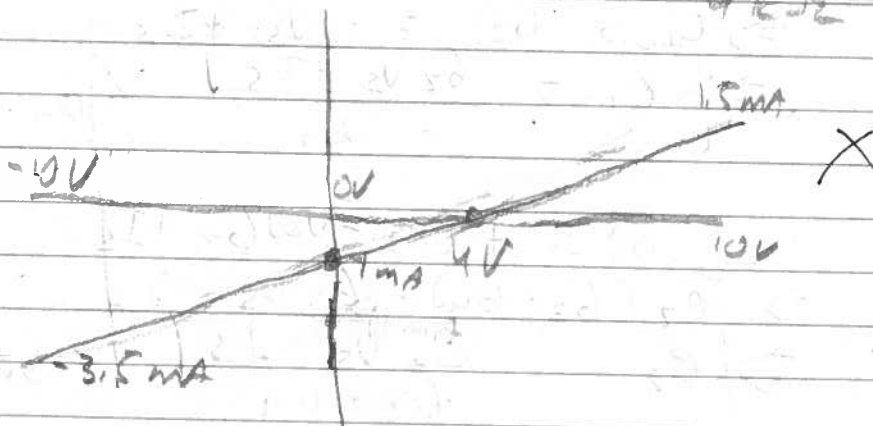$(V_s - 4\text{V}) = i(4\text{k}\Omega)$   
 $i = \frac{V_s - 4\text{V}}{4\text{k}\Omega}$



$$(e - V_1)G_1 + (e - V_2)G_3 + (e - 0)G_2 = 0$$

$$e(G_1 + G_2 + G_3) = V_2 G_3 + V_1 G_1$$

$$e = \frac{V_2 G_3 + V_1 G_1}{G_1 + G_2 + G_3} \quad \text{where } G_n = 1/R_n$$


↳ Consider  $V_1$  only;  $V_2$  is shorted.  
 $(e' - V_1)G_1 + e'G_2 + e'G_3 = 0$   
 $\Rightarrow e'(G_1 + G_2 + G_3) = V_1 G_1 \Rightarrow e' = \frac{V_1 G_1}{G_1 + G_2 + G_3}$

Next, with  $V_2$  only,  $V_1$  is shorted  
 $(e'' - V_2)G_3 + e''G_2 + e''G_1 = 0$   
 $\Rightarrow e''(G_1 + G_2 + G_3) = V_2 G_3 \Rightarrow e'' = \frac{V_2 G_3}{G_1 + G_2 + G_3}$

X 7.4.6 (cont)

$$e = e' + e'' = \frac{V_1 G_1 + V_2 G_2}{G_1 + G_2 + G_3} \quad \left( G_n = \frac{1}{R_n} \right)$$

This result is the same as part a.

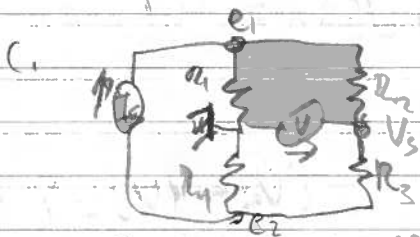

$$(e_1 - 0)G_1 + (e_1 - V_3)G_2 - I_3 = 0$$

$$\Rightarrow e_1(G_1 + G_2) = G_2 V_3 + I_3$$


$$\Rightarrow e_1 = \frac{G_2 V_3 + I_3}{G_1 + G_2} \quad \left( G_n = \frac{1}{R_n} \right)$$

$$(e_2 - 0)G_4 + (e_2 - V_3)G_3 + I_3 = 0$$

$$\Rightarrow e_2(G_3 + G_4) = G_3 V_3 - I_3$$

$$\Rightarrow e_2 = \frac{G_3 V_3 - I_3}{G_3 + G_4} \quad \left( -G_n = \frac{1}{R_n} \right)$$

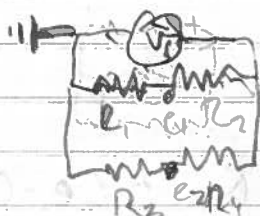Assume  $I_3 = 0 \Rightarrow$  open circuit



The voltage across each branch is simply  $V_3$ .  
 $V_3$  is a voltage divider  
 relation:

other voltage source  $R_1, R_2, R_3, R_4$

$$e_1' = \frac{V_3 R_1}{R_1 + R_2} \quad e_2' = \frac{V_3 R_3}{R_3 + R_4}$$

$V_3$  is a voltage divider

$V_3$  is a voltage divider


$V_3$  is a voltage divider

$V_3$  is a voltage divider

4d cont

Now consider  $V_s = 0$

is short circuit

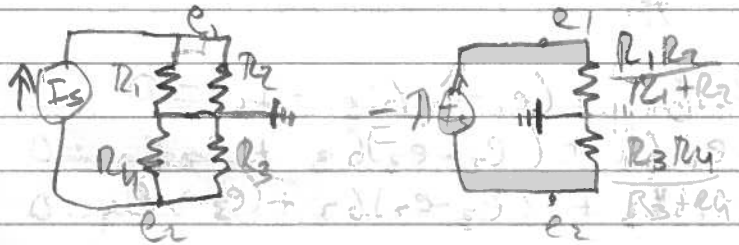


$$e_1'' = \frac{R_1 R_2 I_s}{R_1 + R_2}, \quad e_2'' = -\frac{R_3 R_4 I_s}{R_3 + R_4}$$

$$e_1 = e_1' + e_1'' = \frac{V_s R_1 + R_1 R_2 I_s}{R_1 + R_2} \quad \left( = \frac{V_s G_2 + I_s}{G_1 + G_2} \text{ as in part c} \right)$$

$$e_2 = e_2' + e_2'' = \frac{V_s R_4 - I_s R_3 R_4}{R_3 + R_4} \quad \left( = \frac{V_s G_3 - I_s}{G_3 + G_4} \text{ as in part c} \right)$$

2) S

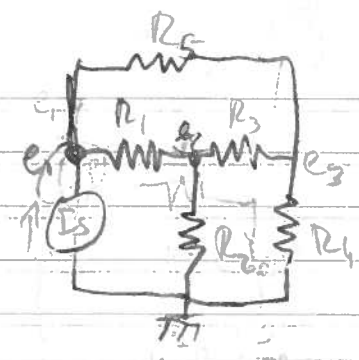

a.

$$\begin{aligned}
 (e_1 - e_2)G_1 + (e_1 - e_3)G_5 - I_s &= 0 \\
 (e_2 - e_1)G_1 + (e_2 - e_3)G_3 + e_2 G_2 &= 0 \\
 (e_3 - e_1)G_5 + (e_3 - e_2)G_3 + (e_3 - e_0)G_4 &= 0
 \end{aligned}$$

$$\begin{aligned}
 e_1(G_1 + G_5) - e_2 G_1 - e_3 G_5 &= -I_s \\
 -e_1 G_1 + e_2(G_1 + G_3 + G_2) - e_3 G_3 &= 0 \\
 -e_1 G_5 - e_2 G_3 + e_3(G_3 + G_4 + G_5) &= 0
 \end{aligned}$$

$$\begin{bmatrix} G_1 + G_5 & -G_1 & -G_5 \\ -G_1 & G_1 + G_2 + G_3 & -G_3 \\ -G_5 & -G_3 & G_3 + G_4 + G_5 \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \\ e_3 \end{bmatrix} = \begin{bmatrix} -I_s \\ 0 \\ 0 \end{bmatrix}$$

b.

$$\begin{bmatrix} 2 & -1 & -1 \\ -1 & 3 & -1 \\ -1 & -1 & 3 \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \\ e_3 \end{bmatrix} = \begin{bmatrix} -I_s \\ 0 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} e_1 \\ e_2 \\ e_3 \end{bmatrix} = \begin{bmatrix} 1/2 & 1/8 & 1/8 \\ 1/2 & 3/8 & 1/8 \\ 1/2 & 3/8 & 5/8 \end{bmatrix} \begin{bmatrix} -I_s \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} -I_s/10 \\ -I_s/20 \\ -I_s/20 \end{bmatrix}$$

c. The Thevenin-equivalent resistance \$R\_{th}\$ can be found by applying a test current and finding the voltage required. From above, if a current \$I\_s\$ is applied, then a voltage \$I\_s/10 = I\_s \cdot 1\Omega\$ is measured across the terminals of the source. Thus \$R\_{th} = V/I = I\_s \cdot 1\Omega / I\_s\$

**$= 1\Omega$**