

Dan Ports  
61002 PSE

6/10

1.A.  $I_{DS} = k/2 (V_{GS} - V_T)^2$

At a few points on the graph, this gives

$5 \text{ mA} = k/2 (3V - V_T)^2$

$2 \text{ mA} = k/2 (4V - V_T)^2$

$4.5 \text{ mA} = k/2 (8V - V_T)^2$

These equations are satisfied by

$V_T = 2V, k/2 = 1/2 \Rightarrow k = 1 \text{ mA/V}^2$

B. For a,  $V_{GS} = 0, V_D = V_S - I_{DS} R_1$

$\Rightarrow V_{DS} = -V_S - I_{DS} R_1$

For b,  $V_{GS} = I_{DS} R_2, V_D = V_S$

$\Rightarrow V_{DS} = V_S - I_{DS} R_2$

For c,  $V_{GS} = I_{DS} R_2, V_D = V_S - I_{DS} R_1$

$\Rightarrow V_{DS} = V_S - I_{DS} R_1 - I_{DS} R_2$

See attached graphs.

C. For a,  $V_{GS} = V_{DS}, V_I = V_{GS}$

$1/R_1 (V_S - V_{DS}) = k/2 (V_{GS} - V_T)^2$

$\Rightarrow V_S - V_0 = R_1 k/2 (V_I - V_T)^2$

$\Rightarrow V_0 = V_S - \frac{R_1 k}{2} (V_I - V_T)^2$

For b,  $V_0 = I_{DS} R_2 = V_S - V_{DS}$

$V_I = V_S - V_{DS} + V_{GS} \Rightarrow V_{GS} = V_I - (V_S - V_0) = V_I - V_0$

$1/R_2 (V_S - V_{DS}) = k/2 (V_{GS} - V_T)^2$

$\Rightarrow V_0 = R_2 k/2 (V_I - V_0 - V_T)^2$

$V_0 = R_2 k/2 [(V_I - V_T)^2 - 2V_0 (V_I - V_T) + V_0^2]$

$V_0 = R_2 k/2 (V_I - V_T)^2 - R_2 k V_0 (V_I - V_T) + \frac{R_2 k}{2} V_0^2$

$\frac{2V_0}{R_2 k} = (V_I - V_T)^2 - 2(V_I - V_T)V_0 + V_0^2$

$V_0^2 - 2(V_I - V_T)V_0 + \frac{2}{R_2 k} V_0 = -(V_I - V_T)^2$

$V_0^2 - 2(V_I - V_T + 1/R_2 k)V_0 + (V_I - V_T)^2 = 0$

$V_0 = (V_I - V_T + 1/R_2 k) \pm \sqrt{(V_I - V_T + 1/R_2 k)^2 - (V_I - V_T)^2}$

any

1c. For  $C_1$  let  $\beta \in \mathbb{R} - \mathbb{R}_2$  and

$$V_0 = V_S - CR$$

$$V_I = V_0 + CR \Rightarrow V_0 = V_I - CR$$

$$\frac{1}{R_2} (V_S - V_0)^2 - \frac{1}{R_2} (V_0 - V_I)^2$$

$$\frac{1}{R_2} (V_S - V_0 + V_0 - V_I)^2$$

$$\frac{1}{R_2} (V_S - V_I + CR - CR)^2$$

$$\frac{1}{R_2} (V_S - V_I + CR - CR)^2 - 2(V_S - V_I)CR + C^2R^2$$

$$C^2R^2 - 2C(V_S - V_I)R + (V_S - V_I)^2 = 0$$

$$C = \frac{R_2(V_S - V_I) \pm \sqrt{(V_S - V_I)^2 R_2^2 - (V_S - V_I)^2 R_2^2}}{2R_2}$$

$$C = \frac{(V_S - V_I) \pm \sqrt{(V_S - V_I)^2 R_2^2 - (V_S - V_I)^2 R_2^2}}{2R_2}$$

$$V_0 = (R_1 + R_2) (V_S - V_I) \pm \sqrt{(V_S - V_I)^2 R_2^2 - (V_S - V_I)^2 R_2^2}$$

D. For  $C_2$

$$V_0 = (V_S - V_I) \pm \sqrt{(V_S - V_I)^2 R_2^2 - (V_S - V_I)^2 R_2^2}$$

For small signal gain,  $\beta \approx 1$  can be neglected.

Then the radical term drops out and

$$V_0 = (V_S - V_I)$$

$\frac{dV_0}{dV_I} = 1$

For  $C_3$

$$V_0 = (R_1 + R_2) (V_S - V_I) \pm \sqrt{(V_S - V_I)^2 R_2^2 - (V_S - V_I)^2 R_2^2}$$

Similarly, the radical term drops out

$$V_0 = (R_1 + R_2) (V_S - V_I)$$

For  $V_1 < V_0$

$$\Rightarrow V_1 < V_1 < V_0 + V_1$$

For  $V_1 < V_0$

$$\Rightarrow V_1 < V_1 - V_0 < V_0 - V_0$$

For  $V_1 < V_0$

$$\Rightarrow V_1 < V_1 - R_2 \left( \frac{V_0}{R_1 + R_2} \right) < V_0 - R_2 \left( \frac{V_0}{R_1 + R_2} \right)$$

check this!

3

$$V_1 = \frac{V_0 R_2}{R_1 + R_2}$$

$$V_1 < V_0 \Rightarrow \frac{V_0 R_2}{R_1 + R_2} < V_0$$

$$\Rightarrow R_2 < R_1 + R_2$$

$$\Rightarrow 0 < R_1$$

2. A. Assume all MOSFETS are in saturation

Then  $2 \text{ mA} = I_{D3} = \frac{k}{2} (V_{GS3} - V_{T3})^2$

$\rightarrow 4 \text{ mA} = \frac{1 \text{ mA}}{2} (V_{GS3} - 2 \text{ V})^2$

$4 = (V_{GS3} - 2 \text{ V})^2 \Rightarrow V_{GS3} - 2 \text{ V} = 2 \Rightarrow V_{GS3} = 4 \text{ V}$

By the voltage divider relation,

$V_{GS3} = \frac{20 \text{ V} \cdot R}{8 \text{ k}\Omega + R} = 4 \text{ V}$

$\rightarrow 20 \text{ V} \cdot R = 8 \text{ k}\Omega \cdot 4 \text{ V} + R \cdot 4 \text{ V}$

$\rightarrow 16 \text{ V} \cdot R = 32 \text{ k}\Omega \cdot \text{V}$

$\Rightarrow R = 2 \text{ k}\Omega$

B.  $I_A + I_B = I_C$  The two MOSFETS have the same characteristics and gate voltages.

So  $I_A = I_B \Rightarrow 2 I_A = I_C = 2 \text{ mA} \Rightarrow I_A = 1 \text{ mA}$

$I_{D1} = I_A = \frac{k}{2} (V_{GS1} - V_{T1})^2 \Rightarrow \frac{2 \text{ mA}}{2 \text{ V}^2} (0 - E_x - 2 \text{ V})^2$

$\Rightarrow 1 \text{ V}^2 = (-E_x - 2 \text{ V})^2 \Rightarrow E_x = -3 \text{ V}$

$I_A = I_B = 1 \text{ mA}$

C.  $I_A + I_B = 2 \text{ mA}$

$\Rightarrow \frac{2 \text{ mA}}{2 \text{ V}^2} (V_1 - E_x - 2 \text{ V})^2 + \frac{2 \text{ mA}}{2 \text{ V}^2} (-E_x - 2 \text{ V})^2 = 2 \text{ mA}$

$\Rightarrow (V_1 - E_x - 2 \text{ V})^2 + (-E_x - 2 \text{ V})^2 = 2 \text{ V}^2$

Using a linear approximation

$(V_1 - E_x - 2 \text{ V})^2 + 2(-E_x - 2 \text{ V})(V_1 - E_x) +$

$(-E_x - 2 \text{ V})^2 + 2(-E_x - 2 \text{ V})(-E_x) \approx 2 \text{ V}^2$

$\Rightarrow 2(-E_x - 2 \text{ V})(V_1 - E_x) + 2(-E_x - 2 \text{ V})(-E_x) \approx 0$

$\Rightarrow (V_1 - E_x) + (-E_x) \approx 0 \Rightarrow V_1 - 2 E_x \approx 0$


$\Rightarrow E_x \approx -V_1/2$

$V_0 = 10 \text{ V} - I_B \cdot 5 \text{ k}\Omega \approx 10 \text{ V} - 5 \text{ k}\Omega \cdot \frac{1 \text{ mA}}{1 \text{ V}^2} (E_x - 2 \text{ V})^2$

Using a linear approximation,

$V_0 = \frac{dV_0}{dE_x} E_x \cdot e_x$

3A

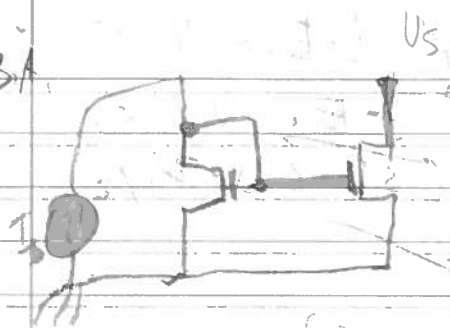

Consider the first MOSFET.  
 $I_s$  must satisfy the relation  
 $I_s = \frac{k}{2} (V_{GS} - V_T)^2$   
 The current flowing in  
 $I_s = I_{S1} = I_{S2}$   
 $I_s = \frac{k}{2} (V_{GS} - V_T)^2$

We can solve for  $V_{GS}$

$$I_s \cdot \frac{2}{k} = (V_{GS} - V_T)^2$$

$$\Rightarrow V_{GS} = \sqrt{I_s \cdot \frac{2}{k}} + V_T$$

The second MOSFET has the same gate voltage and characteristics, so we can solve for its current,  $I_o$ .

$$I_o = \frac{k}{2} (V_{GS} - V_T)^2 = \frac{k}{2} (\sqrt{I_s \cdot \frac{2}{k}} + V_T - V_T)^2$$

$$I_o = \frac{k}{2} (\sqrt{I_s \cdot \frac{2}{k}})^2 = \frac{k}{2} \cdot I_s \cdot \frac{2}{k}$$

$$I_o = I_s$$

①

The output current is equal to the input current; it mirrors it.

B. There is no change. The same current  $I_o = I_s$  flows through the resistor.

$$V_o = \frac{dV_o}{d e_x} \Big|_{E_x} \cdot e_x = -5k\Omega \cdot \frac{1mA}{\sqrt{2}} (-E_x - 2V) \cdot (-1) \cdot e_x$$

$$= \frac{10k\Omega \cdot mA}{\sqrt{2}} (-E_x - 2V) e_x$$

$$= 10 \mu V \cdot (3V - 2V) \cdot \sqrt{2}/2$$

$$V_o = 5 \mu V$$

$$\Rightarrow V_o / V_i = 5$$

D.  $M_2$  will cut off when  $V_{GS2} < V_T \Rightarrow (0 - E_x) < 2V$

From above,  $(V_i - e_x - 2V)^2 + (-e_x - 2V)^2 = 2V^2$

$$\Rightarrow e_x^2 - 2e_x(V_i + 2V) + (V_i - 2V)^2 + e_x^2 + 2e_x \cdot 2V + 4V^2 = 2V^2$$

$$\Rightarrow 2e_x^2 - 2e_x(V_i + 2V) + (V_i - 2V)^2 + 4V^2 = 2V^2$$

$$\Rightarrow 2e_x^2 - 2e_x V_i - 2e_x \cdot 2V + V_i^2 - 2V \cdot V_i + 4V^2 - 2V^2 = 0$$

$$e_x = \frac{2V_i + \sqrt{4V_i^2 - 8V_i \cdot 2V + 16V^2}}{4}$$

$$e_x = \frac{2V_i \pm \sqrt{4V_i^2 - 16V_i \cdot 2V + 16V^2}}{4}$$

$$= \frac{1}{2} V_i \pm \sqrt{V_i^2 - 4V_i \cdot 2V + 4V^2}$$

Since  $-e_x < 2V$  is the cutoff,

$$\frac{1}{2} V_i \pm \sqrt{V_i^2 - 4V_i \cdot 2V + 4V^2} \rightarrow -2V$$

leads to the cutoff

$$V_i = \sqrt{2} V$$

