

Damn Ports
6.002 PS6

9/10 ~~10~~

1.a. $V_A = 10V - I_D \cdot 5k\Omega$

For cutoff, $V_A = 10V$ for $V_{in} < V_T \Rightarrow V_{in} < 2V$

In saturation:

$$V_A = 10V - 5k\Omega \left(\frac{2mA}{\sqrt{2}} \cdot \sqrt{V_{in} - 2V} \right)^2$$

$$= 10V - 5V \cdot (V_{in} - 2V)^2 / 1V = 10V - 5(V_{in} - 2V)^2$$

for $V_{in} > V_T \Rightarrow V_{in} > 2V$

and $V_{DS} > V_{DS} - V_T \Rightarrow 10V - 5(V_{in} - 2V)^2 > V_{in} - 2V$

$$\Rightarrow 10V - 5V_{in}^2 + 20V_{in} - 20V > V_{in} - 2V$$

$$5V_{in}^2 / 1V - 20V_{in} + 10V < 2V - V_{in}$$

$$5V_{in}^2 / 1V - 19V_{in} + 8V < 0$$

$$\Rightarrow V_{in} < 3.3177V$$


In triode,

$$V_A = 10V - 5k\Omega \left(\frac{2mA}{\sqrt{2}} \cdot \sqrt{V_A} \right)^2$$

$$\Rightarrow V_A = 10V - 5V_A^2 / 1V \Rightarrow 5V_A^2 / 1V + V_A - 10V = 0$$

$$\Rightarrow V_A = 1.3177V$$

for $V_{in} > 3.3177V$

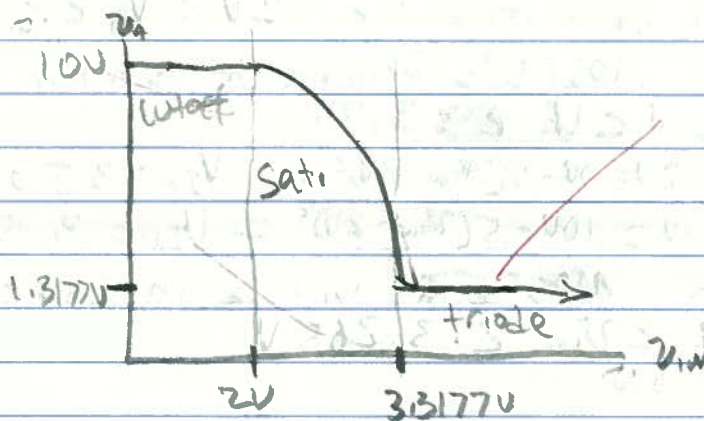


2.16 b) By the symmetry of the circuit, the $V_0 - V_A$ relation is the same as the $V_A - V_I$ relation.

Thus $V_0 = 10V$ for $V_A < 2V$ (cut-off) $V_0 = 10V - 5(V_A - 2V)^2$ (sat)

is $V_0 = 1.3177V$ for $V_A > 2V$ and $V_A < 3.3177V$

$V_0 = 1.3177V$ for $V_A > 3.3177V$

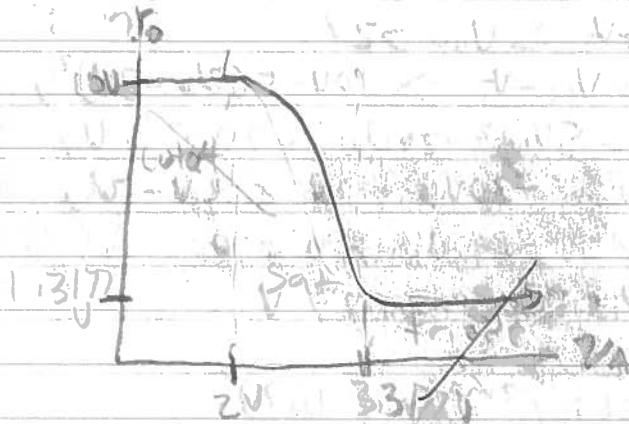

M_1 will be in saturation for $1.3177V < V_A < 10V$

M_2 will be in saturation for $2V < V_A < 3.3177V$

Thus both MOSFETS will be in saturation when $2V < V_A < 3.3177V$

$$V_A = 2V \Rightarrow 2V = 10V - 5(V_{in} - 2V)^2 \Rightarrow V_{in} = 3.265V$$

$$V_A = 3.3177V = 10V - 5(V_{in} - 2V)^2 \Rightarrow V_{in} = 3.156V$$

Thus both MOSFETS will be in saturation at $3.156V < V_{in} < 3.265V$

$$\begin{aligned} d) \quad V_0 &= 10V - 5(V_A - 2V)^2 \\ &= 10V - 5((10V - 5(V_{in} - 2V)^2) - 2V)^2 \\ &= -125V_{in}^4/V^3 + 1000V_{in}^3/V^2 - 2600V_{in}^2/V \\ &\quad + 2400V_{in} - 710 \end{aligned}$$

e. Let $v_{i1} = 3.2V + v_i$, $v_o = V_o + v_o$

Then $v_o = \frac{dV_o}{dV_i} \cdot v_i$

$$v_o = (-500V/V) + 3000V/V^2 - 5200V/V + 24000V/V^2$$

$$= (-16800 + 30720 - 16640 + 24000) V/V$$

$$= 96 V/V$$

$\frac{v_o}{v_i} = 96$




$$v_a = k(V_{GS} - V_T) v_{GS} \cdot 5k\Omega + A$$

$$= \frac{2mA}{V^2} (3.2V - 2V) v_i \cdot 5k\Omega$$

$$= 12V/V (1.2V) v_i$$

$$= 14.4 v_i$$

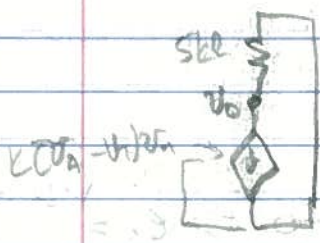

$$v_o = k(V_{GS} - V_T) v_a \cdot 5k\Omega$$


$$= \frac{2mA}{V^2} (2.8V - 2V) v_a \cdot 5k\Omega$$

$$= 8V/V (1.2V) v_a$$

$$= 9.6 v_a$$

2

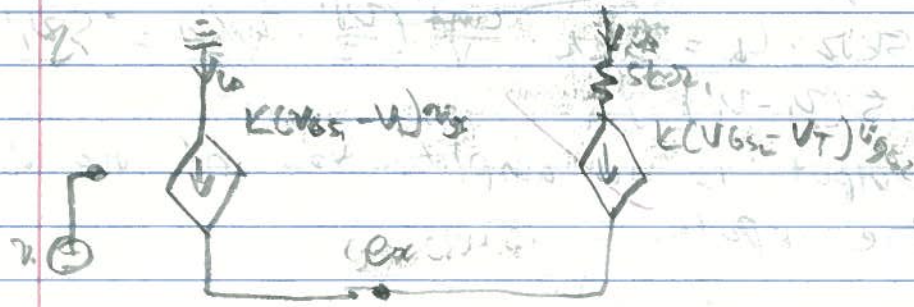$\frac{v_o}{v_i} = 96$, same gain as above



The bias voltage at the common source of M_1 and M_2

is $3V = V_{GS} = V_{GS} + v_{GS}$

$$I_{D1} = \frac{2mA}{V^2} (3V - 2V) (V_{GS} - v_{GS})$$

$$I_{D2} = \frac{2mA}{V^2} (3V - 2V) (0 - v_{GS})$$

$$I_a + I_b = 0 \Rightarrow v_1 - e_x - e_x = 0 \Rightarrow e_x = \frac{1}{2} v_1$$

$$I_b = \frac{2mA}{\sqrt{2}} (3V - 2V) (0 - e_x) = \frac{2mA}{\sqrt{2}} (-\frac{1}{2} v_1) =$$

$$v_o = 5k\Omega \cdot I_b = 5k\Omega \cdot \left(-\frac{1}{2} v_1 \cdot \frac{2mA}{\sqrt{2}}\right) = -5v_1$$

$$\Rightarrow \boxed{\frac{v_o}{v_1} = -5}$$

$$c. I_a = \frac{2mA}{\sqrt{2}} (1V) (-e_x)$$

$$I_b = \frac{2mA}{\sqrt{2}} (1V) (v_1' - e_x)$$

$$I_a + I_b = 0 \Rightarrow v_1' - e_x - e_x = 0 \Rightarrow v_1' - 2e_x \Rightarrow e_x = \frac{v_1'}{2}$$

$$I_b = \frac{2mA}{\sqrt{2}} \cdot 1V \cdot \left(\frac{v_1'}{2} - \frac{v_1'}{2}\right) = \frac{2mA}{\sqrt{2}} \left(\frac{v_1'}{2}\right)$$

$$v_o = -5k\Omega \cdot I_b = -5k\Omega \cdot \frac{2mA}{\sqrt{2}} \cdot \frac{v_1'}{2} = -5v_1'$$

$$\Rightarrow \boxed{\frac{v_o}{v_1'} = -5}$$

$$d. I_a = \frac{2mA}{\sqrt{2}} (1V) (v_1 - e_x)$$

$$I_b = \frac{2mA}{\sqrt{2}} (1V) (v_1' - e_x)$$

$$I_a + I_b = 0 \Rightarrow v_1 - e_x + v_1' - e_x = 0 \Rightarrow e_x = \frac{v_1 + v_1'}{2}$$

$$I_b = \frac{2mA}{\sqrt{2}} \cdot 1V \cdot \left(v_1' - \frac{v_1 + v_1'}{2}\right) = \frac{2mA}{\sqrt{2}} \left(\frac{v_1' - v_1}{2}\right)$$

$$v_o = 5k\Omega \cdot I_b = 5k\Omega \cdot \frac{2mA}{\sqrt{2}} \left(\frac{v_1' - v_1}{2}\right) = 5v_1' - 5v_1$$

$$\boxed{v_o = 5(v_1' - v_1)}$$


The output is an amplification of the difference of the inputs.

3.a.

$$C_1 + \frac{L_2(L_3 + C_4)}{L_2 + L_3 + C_4} = \cancel{\text{seen}}$$


b.
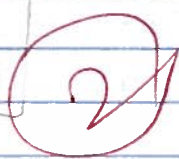
$$L_1 + \frac{L_2(L_3 + L_4)}{L_2 + L_3 + L_4} = \cancel{\text{seen}}$$



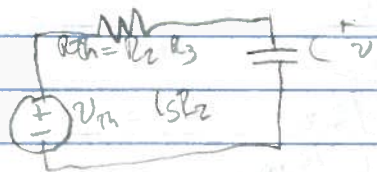4.a.

Replace network 1 w/ Thevenin eq. v. across the capacitor.



At time 0+, the capacitor is a short circuit. $V(0+) = 0$

At time ∞ , the capacitor is an open circuit. $V(\infty) \rightarrow V_m = I_{sc} R_2$

Replace network 2 w/ Norton eq.



At time 0+, the inductor allows no current flow. $I(0+) = 0$

At time ∞ , the inductor is a short circuit. $I(\infty) \rightarrow I_{sc} = V_1/R_1 - V_2/R_2$

b. The circuits have time constants $\tau = L / (R_1 + R_2)$ and $V_m = L \cdot I_{sc} = L \cdot (V_1/R_1 - V_2/R_2)$

c. $V(t) = I_{sc} R_2 - I_{sc} R_2 e^{-t / (R_1 + R_2)}$

$$V(t) = \left(\frac{V_1}{R_1} - \frac{V_2}{R_2} \right) R_2 e^{-t / (R_1 + R_2)}$$


ignore

d. The current $i(0^-)$ at time zero is the current due to v_2 only: $i(0^-) = \frac{v_2}{R_2}$. This is also the current $i(0^+)$ because the inductor resists change. $i(\infty)$ is as before, $\frac{v_1}{R_1} - \frac{v_2}{R_2}$.

Thus the current $i(t)$ is $\frac{v_2}{R_2} + \frac{v_1}{R_1} e^{-t/\tau}$


$$i(t) = \frac{v_2}{R_2} + \frac{v_1}{R_1} \left(1 - e^{-t/\tau}\right)$$

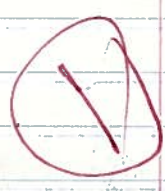e) At $t=0^-$, $i_{R_2} = v_2/R_2$
 at $t=0^+$, $i_{R_2} = v_1/R_1 + v_2/R_2$
 at $t=\infty$, $i_{R_2} = v_2/R_2$



$$i_{R_2}(t) = \frac{v_2}{R_2} + \frac{v_1}{R_1} e^{-t/\tau}$$

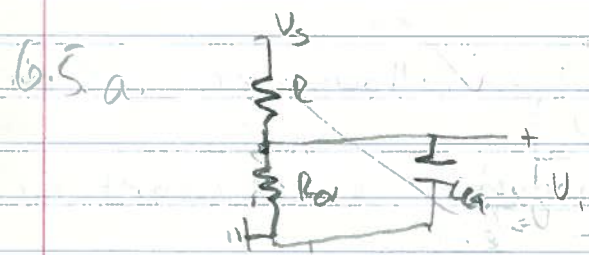(where τ is the time constant from above)




$$v(0^+) = v_s \frac{R_0}{R + R_0} \approx 0$$

because $R \gg R_0$

$$\tau = (R \parallel R_0) C_0 \approx R_0 C_0$$


because $R_0 \ll R$.

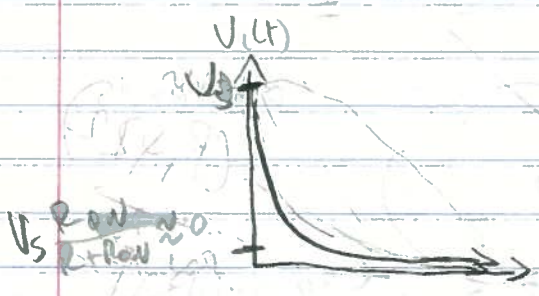

$$v(t) = v_s \frac{R_0}{R + R_0} \left(1 - e^{-t/\tau}\right)$$

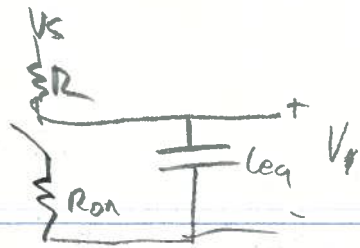b) $v_{0L} = v_s \left(1 - e^{-t/\tau}\right) \Rightarrow \frac{v_{0L}}{v_s} = 1 - e^{-t/\tau}$

$$\Rightarrow \ln \frac{v_{0L}}{v_s} = -\frac{t}{\tau} \Rightarrow t = -\tau \ln \left(\frac{v_{0L}}{v_s}\right)$$




$$V_v(t=1/2) \approx 0$$

$$V_v(t=0) = V_s$$

$$\tau = RC$$

$$V_v(t) = V_s (1 - e^{-t/RC})$$

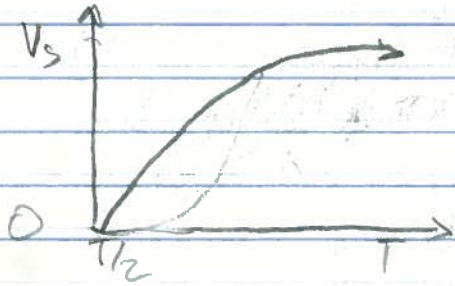

$$V_{OH} = V_s (1 - e^{-t/RC})$$


$$\frac{V_{OH}}{V_s} = 1 - e^{-t/RC} \Rightarrow e^{-t/RC} = 1 - \frac{V_{OH}}{V_s} \quad (R_{in} + R)$$

$$\Rightarrow \frac{-t}{RC} = \ln\left(1 - \frac{V_{OH}}{V_s}\right) \Rightarrow t = -RC \ln\left(1 - \frac{V_{OH}}{V_s}\right)$$

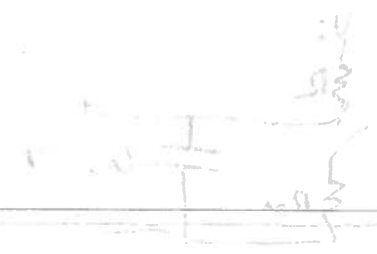
d. Reducing R can allow faster switching times, but it also causes the output low voltage, $V_s \left(\frac{R_{OH}}{R+R_{OH}}\right)$, to increase.



Handwritten notes at the top left, possibly including a date or page number.




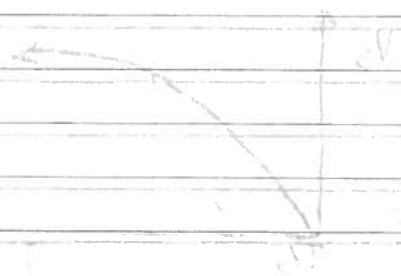Handwritten text and a shaded area, possibly a title or a section header.



Handwritten text, possibly a label or a description of the diagram above.

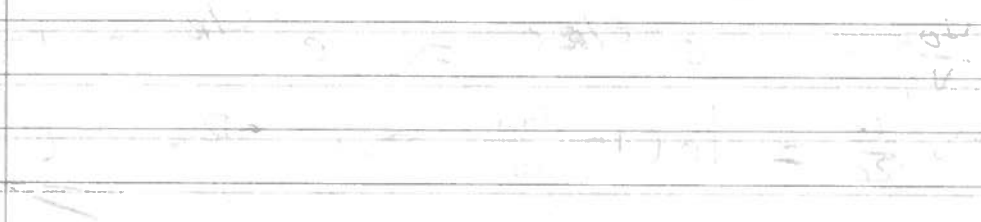Handwritten text on the left margin, possibly a page number or a reference.



Handwritten text, possibly a title or a section header, with a curved arrow pointing downwards.

A circled number '11' in the lower right quadrant of the page.