

JC $\frac{10}{10}$

Don Ports
6002 PS 8

2) a. At $t=0$, $v(0) = 0$ by continuity
As $t \rightarrow \infty$, $v(\infty) \rightarrow V/R_1$

$$v(t) = \frac{V_s}{R_1} (1 - e^{-t/\tau}), \quad \tau = \frac{L}{R_1 + R_2}$$

$$i(t) = -L \frac{dv(t)}{dt} = \frac{V_s R_2}{R_1 + R_2} e^{-t/\tau} u(t)$$

$$v_{oa} = \frac{V_s R_2}{R_1 + R_2} e^{-t/\tau} u(t), \quad \tau = \frac{L(R_1 + R_2)}{R_1 R_2}$$

$$b. v_{sb} = \int_{-\infty}^t v_{sa}(t') dt'$$

$$\Rightarrow v_{ob} = \int_{-\infty}^t v_{ob}(t') dt'$$

$$= \int_{-\infty}^t \frac{V_s R_2}{R_1 + R_2} e^{-t'/\tau} u(t') dt'$$

$$= \frac{V_s R_2 \tau}{R_1 + R_2} e^{-t'/\tau} \Big|_0^t u(t)$$

$$= \frac{V_s R_2 \tau}{R_1 + R_2} (e^{-t/\tau} - 1) u(t)$$

$$= \frac{V_s R_2 (L(R_1 + R_2))}{R_1 + R_2 R_1 R_2} (1 - e^{-t/\tau}) u(t)$$

$$v_{ob} = \frac{V_s L}{R_1} (1 - e^{-t/\tau}) u(t) \quad \checkmark$$

$$c. v_{oc}(t) = v_{ob}(t) - v_{ob}(t - T)$$

$$\text{by linearity, } v_{oc}(t) = v_{ob}(t) - v_{ob}(t - T)$$

$$= \frac{V_s L}{R_1} \left[(1 - e^{-t/\tau}) u(t) - e^{-(t-T)/\tau} u(t-T) \right]$$

$\frac{0}{0}$ 0T

d. $v_{sd}(t) = v_{sc}(t) + v_{sa}(t)$

$\Rightarrow v_{od}(t) = v_{oc}(t) + v_{oa}(t)$

$v_{od}(t) = 1V \cdot \frac{R_2}{R_1 + R_2} (e^{-t/\tau}) u(t)$

(S)

$+ 1V \cdot \frac{L}{R_1} \left[(1 + e^{-t/\tau}) u(t) - (1 - e^{-(t-T)/\tau}) u(t-T) \right]$

e. $v_{sc}(t) = v_{sd}(t) - v_{sc}(t-2T) + v_{sa}(t-3T)$

$\Rightarrow v_{oc}(t) = v_{oc}(t) - v_{oc}(t-2T) + v_{oa}(t-3T)$

$v_{oc}(t) = 1V \cdot \frac{R_2}{R_1 + R_2} (e^{-t/\tau}) u(t)$

$+ 1V \cdot \frac{L}{R_1} \left[(1 - e^{-t/\tau}) u(t) - (1 - e^{-(t-T)/\tau}) u(t-T) \right]$

$- 1V \cdot \frac{L}{R_1} \left[(1 - e^{-(t-2T)/\tau}) u(t-2T) \right]$

$- (1 - e^{-(t-3T)/\tau}) u(t-3T)]$

$- 1V \cdot \frac{R_2}{R_1 + R_2} e^{-\frac{(t-3T)}{\tau}} u(t-3T)$

2

2a. During the first half-period the capacitor (C) discharges from V_s to $V_{L0} = V_s \frac{R_{ow}}{R+R_{ow}}$. The change in energy stored in the capacitor is

$$\Delta E_C = \frac{1}{2} C V_s^2 - \frac{1}{2} C \left(V_s \frac{R_{ow}}{R+R_{ow}} \right)^2$$

The energy dissipated is equal to this energy plus the integral of the static power over time $T/2$

$$E_{dissipated} = \frac{1}{2} C \left[V_s^2 - \left(V_s \frac{R_{ow}}{R+R_{ow}} \right)^2 \right] + \frac{V_s^2}{(R+R_{ow})} \frac{T}{2}$$

almost

b. During the second period, the voltage source charges the capacitor and dissipates energy through the resistors. So $E_{supplied} = E_{dissipated} + E_{stored}$.

$$\begin{aligned} E_{supplied} &= \int_{T/2}^T P_{supplied} dt = \int_{T/2}^T V_s I dt \\ &= \int_{T/2}^T V_s \frac{(V_s - V_C)}{R} dt = \int_{T/2}^T \left(\frac{V_s^2}{R} - \frac{V_s V_C}{R} \right) dt \\ &= \frac{V_s^2 T}{R} - \frac{V_s}{R} \int_{T/2}^T \left(V_s - \frac{R}{R_{ow} + R} V_s e^{-(t-T/2)/\tau_c} \right) dt \\ &= \frac{V_s^2 T}{R} - \frac{V_s^2 T}{2R} - \frac{V_s^2}{R} \int_0^T \frac{R}{R_{ow} + R} e^{-t/RC} dt \\ &= \frac{V_s^2}{R_{ow} + R} \cdot RC \left(e^0 - e^{-T/RC} \right) \\ &= \frac{V_s^2}{R_{ow} + R} RC \end{aligned}$$

The energy stored in the capacitor is the same as part A, so $E_{dissipated} = E_{supplied} - E_{stored}$

$$E_{ds} = \frac{V_s^2 RC}{R_{ow} + R} - \frac{1}{2} C \left[V_s^2 - \left(V_s \frac{R_{ow}}{R+R_{ow}} \right)^2 \right]$$

very good

c. The time-averaged total power is the energies from part a and b added and divided by T .

$$\begin{aligned} \bar{P} &= \frac{1}{T} \left[\frac{1}{2} C (V_s^2 - \frac{V_s^2 R_{ow}}{R+R_{ow}})^2 + \frac{V_s^2 T}{R+R_{ow}} \right] \\ &= \frac{1}{T} \left[\frac{V_s^2 T}{R+R_{ow}} + \frac{V_s^2 R C_{eq}}{R+R_{ow}} \right] \\ &= \frac{V_s^2}{2(R+R_{ow})} + \frac{V_s^2 R C_{eq}}{(R+R_{ow}) T} \end{aligned}$$

↑ Static
 ↑ dynamic

d. $P = \frac{25V^2}{2.1 + 0.1k\Omega} + \frac{25V^2 \cdot 100k\Omega \cdot 10^{-2}pF}{110k\Omega \cdot 10^{-6}s}$

$= 0.114 \text{ mW}$ (Static) + 0.023 mW (dynamic) = 0.136 mW

Static dominates

②

3 a

A	B	C	Z
L	L	L	H
L	L	H	L
L	H	L	H
L	H	H	L
H	L	L	H
H	L	H	L
H	H	L	L
H	H	H	L

\checkmark AB + C
 \checkmark

done

b

c

d

A	B	C	D	Z
L	L	L	L	H
L	L	L	H	H
L	L	H	L	L
L	L	H	H	H
L	H	L	L	H
L	H	L	H	H
L	H	H	L	L
L	H	H	H	H
H	L	L	L	H
H	L	L	H	H
H	L	H	L	L
H	L	H	H	H
H	H	L	L	L
H	H	L	H	L
H	H	H	L	L
H	H	H	H	H

A	B	C	D	Z
L	L	L	L	H
L	L	L	H	H
L	L	H	L	L
L	L	H	H	H
L	H	L	L	L
L	H	L	H	H
L	H	H	L	L
L	H	H	H	H
H	L	L	L	H
H	L	L	H	H
H	L	H	L	L
H	L	H	H	H
H	H	L	L	L
H	H	L	H	L
H	H	H	L	L
H	H	H	H	H


A	B	C	D	Z
L	L	L	L	L
L	L	L	H	L
L	L	H	L	H
L	L	H	H	L
L	H	L	L	H
L	H	L	H	L
L	H	H	L	H
L	H	H	H	L
H	L	L	L	L
H	L	L	H	L
H	L	H	L	H
H	L	H	H	H
H	H	L	L	H
H	H	L	H	H
H	H	H	L	H
H	H	H	H	H

$Z = AB + CD$



$Z = (A + D)(B + C)$

$Z = (A + D)(B + C)$

2

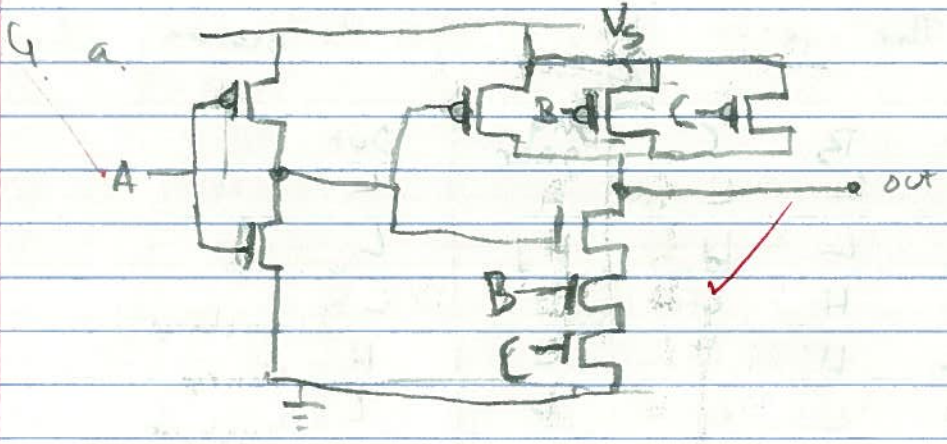

3

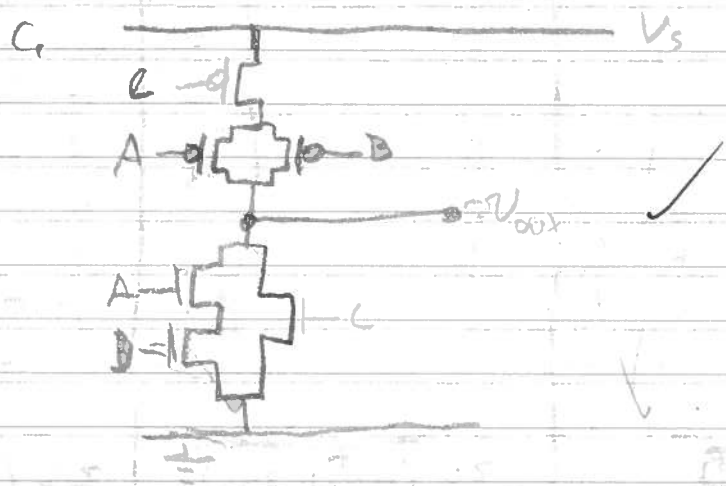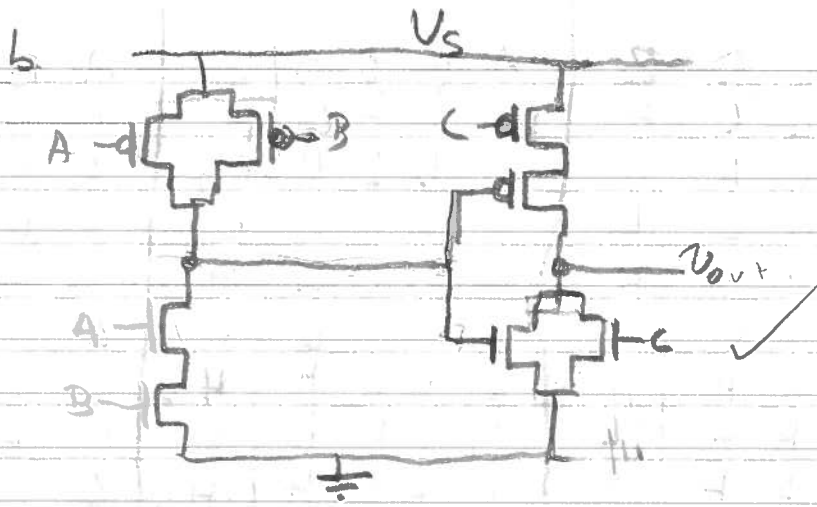

5. The circuit has the following characteristics

A	B	C	majority gate	Out	
L	L	L	L	L	
L	L	H	L	L	
L	H	L	L	L	discharge
L	H	H	H	H	charge
H	L	L	L	L	discharge
H	L	H	H	H	charge
H	H	L	H	L	discharge
H	H	H	H	H	charge

Current is always flowing through one of the R resistors in the steady state because the right branch is the inversion of the left. So there is always a current $V_S / (R + R) = V_S / R$ flowing through one resistor, which means a static power $P = V_S^2 / R$

From the truth table there are 3 L-H transitions in which the capacitor charges and 3 H-L where the capacitor discharges. The energy dissipated while charging to V_S is $1/2 C V_S^2$, and $1/2 C V_S^2$ is lost when discharging.

The total dynamic energy change is

$$3 \cdot 1/2 C V_S^2 + 3 \cdot 1/2 C V_S^2 = 3 C V_S^2$$

The total power is the static power plus the time-average over BT of the dynamic energy change:

$$\overline{P} = \frac{V_S^2}{R} + \frac{3 C V_S^2}{BT}$$

very good.



1. $\frac{1}{x^2} = x^{-2}$

2. $\frac{d}{dx} x^{-2} = -2x^{-3}$

3. $= -2x^{-3}$

4. $= -\frac{2}{x^3}$

5. $= -\frac{2}{x^3}$

6. $= -\frac{2}{x^3}$

7. $= -\frac{2}{x^3}$

8. $= -\frac{2}{x^3}$

9. $= -\frac{2}{x^3}$



loop