


SC

10/10

Dan Ports
6.002 Dsg

3

1. For v_O of ckt,

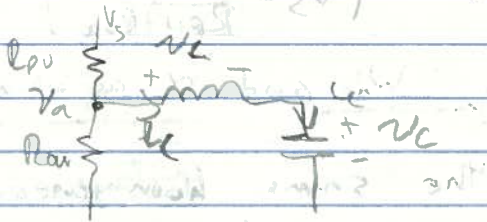

$$v_C(0^-) = 0 \quad v_S$$

$$i_L(0^-) = 0$$

$$v_O = v_C$$

Applying nodal analysis at v_A , we find

$$\frac{(v_A - v_S)}{R_{pu}} + \frac{v_A}{R_{pw}} + i_L = 0 \Rightarrow v_A \left(\frac{1}{R_{pu}} + \frac{1}{R_{pw}} \right) = -i_L + \frac{v_S}{R_{pu}}$$

$$\Rightarrow v_A = \left(i_L + \frac{v_S}{R_{pw}} \right) (R_{pu} \parallel R_{pw})$$

$$\text{Let } R = R_{pu} \parallel R_{pw}$$

$$\text{By KCL, } i_L = i_C; \text{ By KVL, } v_A = v_L + v_C \Rightarrow v_C = v_A - v_L$$

$$\text{From element laws, } i_L = i_C = C \frac{dv_C}{dt}$$

$$\text{and } v_L = L \frac{di_L}{dt} = LC \frac{d^2 v_C}{dt^2}$$

$$v_C = \left[C \frac{dv_C}{dt} + \frac{v_S}{R_{pw}} \right] R - LC \frac{d^2 v_C}{dt^2}$$

$$\Rightarrow i_C + \frac{R i_C v_C}{LC} + \frac{v_C}{LC} = \frac{v_S R}{R_{pw} LC}$$

$$\text{By inspection, the particular soln is } v_C = \frac{v_S R}{R_{pw}}$$

$$D(s) = s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

$$\Rightarrow s = \frac{-R \pm \sqrt{R^2 - 4LC}}{2L} = -\frac{R}{2L} \pm \frac{1}{2L} \sqrt{R^2 - 4LC}$$

$$\text{we know that } \sqrt{L} > R/2 \Rightarrow \frac{L}{C} > R^2/4 \Rightarrow \frac{1}{LC} > \frac{R^2}{4L^2}$$

$$\text{So } s = \frac{-R}{2L} \pm j \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}} = -\alpha \pm j\omega_j$$

$$\left(\text{Let } \omega = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}} \text{ and } \alpha = \frac{R}{2L} \right)$$

The homogeneous response is

$$v_{ch} = e^{-R/2L t} (a \cos \omega t + b \sin \omega t)$$

$$v_c(t) = v_{ce} + v_{ch} = \frac{V_s R_c}{R_{pu}} + e^{-\alpha t} (a \cos(\omega_d t) + b \sin(\omega_d t))$$

The initial conditions $v_c(0) = V_s$ and $i_c(0) = 0$ imply that $a = V_s - \frac{V_s R_c}{R_{pu}}$, $b = 0$

$$v_c(t) = v_c(t) = \frac{V_s R_{ow}}{R_{pu} + R_{ow}} + e^{-\alpha t} \left(V_s - \frac{V_s R_{ow}}{R_{pu} + R_{ow}} \right) \cos(\omega_d t)$$


(for $0 < t < T$; ω_d and α as above, $R = R_{pu} || R_{ow}$)

For $T < t < 2T$, the same homogeneous solution applies, except that no current flows through the MOSFET ($R_{ow} \rightarrow \infty$ and $R_{pu} || R_{ow} = R_{pu}$), and the particular solution and initial conditions are different.

The new particular solution is $v_c(t) = V_s$, and the initial conditions are $v_c(T) = V_s \frac{R_{ow}}{R_{pu} + R_{ow}}$ and $i_c(T) = i_c(0) = 0$.

$$v_c(t) = V_s + \left(\frac{V_s R_{ow}}{R_{pu} + R_{ow}} - V_s \right) e^{-\alpha(t-T)} \cos(\omega_d(t-T))$$

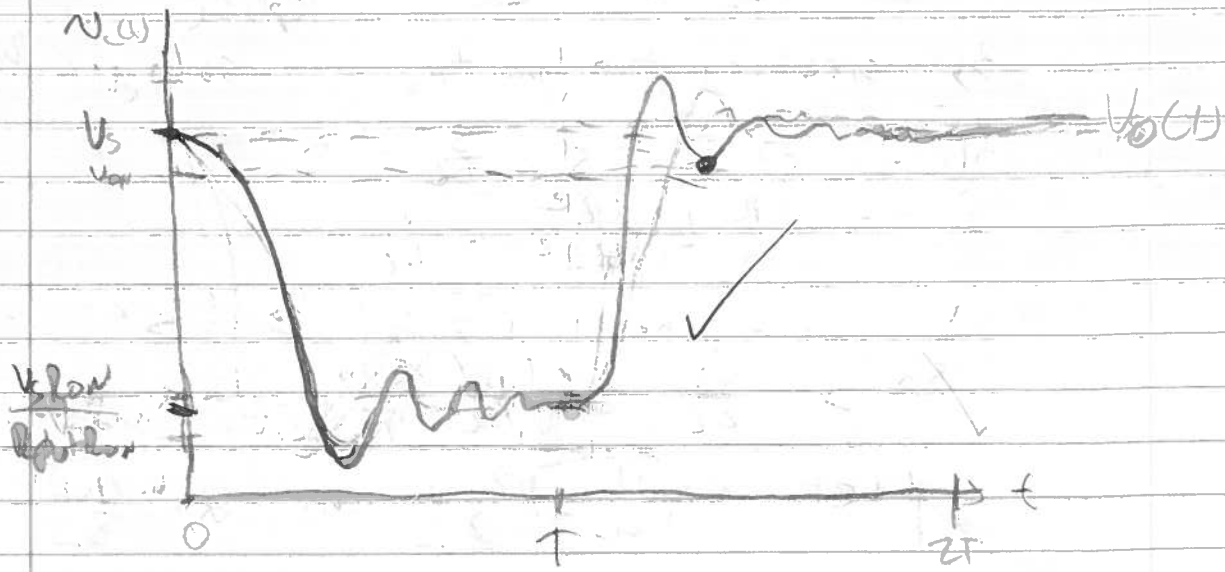for $T < t < 2T$; ω_d and α as above, except $R = R_{pu}$



b. The minimum of $V_o(t)$ after the output switches shifts high must be greater than V_{OH} . This point exists when $\omega_d(t-T) = 2\pi n \Rightarrow$

$t = T + \frac{2\pi n}{\omega_d}$. This point is indicated on the graph. Assuming $R_{out} \ll R_{in}$ and the indicated values.

$$V_o(t) = V_s (1 - e^{-\alpha t}) \cos(\omega_d(t-T))$$

At the minimum point,
 $V_{OH} = 0.8 V_s < V_s (1 - e^{-\alpha T / \omega_d})$

$$\Rightarrow 0.8 < 1 - e^{-2\pi n / \omega_d} \Rightarrow e^{-2\pi n / \omega_d} > 0.2$$


$$\Rightarrow \frac{2\pi n}{\omega_d} > \ln(0.2) \Rightarrow \frac{2\pi R_{in}}{2L \sqrt{1/LC - R_{in}^2}} < -\ln(0.2)$$

$$\Rightarrow \frac{2\pi \cdot 0.1 \cdot 10^3}{2 \cdot L \sqrt{1/L \cdot 10^{-2} - \frac{1 \cdot 10^6}{4L^2}}} < 1.609 \Rightarrow \frac{1}{\sqrt{1/10^{-2} - \frac{1 \cdot 10^6}{4L^2}}} < 0.0005125$$

$$\Rightarrow \frac{L}{10^{-2}} = (250.2)^2 < 3.810 \times 10^6 \Omega^2 \quad \text{close.}$$

$$\Rightarrow \frac{L}{10^{-2}} < 3.873 \times 10^6 \Omega^2 \Rightarrow \boxed{L < 3.873 \times 10^{-8} \text{ H}}$$

2

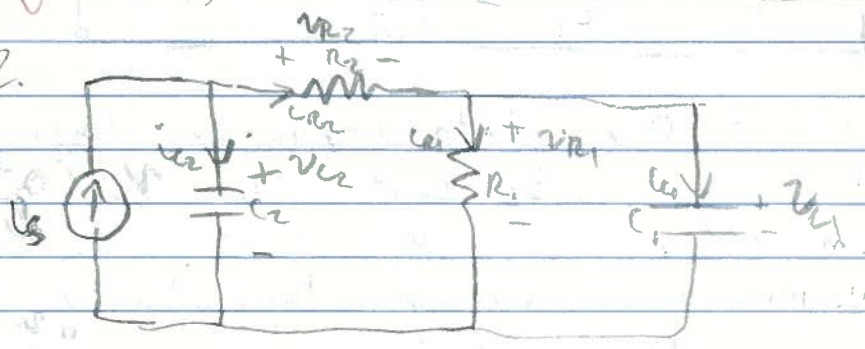

By KCL, $I_s = I_{R2} + I_{C2}$; $I_{C2} = I_{R1} + I_{C1}$

$$I_s = I_{R1} + I_{C1} + I_{C2}$$

$$I_s = \frac{V_{R1}}{R_1} + C_1 \dot{V}_{C1} + \dot{V}_{C2}$$

$$V_{C2} = V_{R2} + V_{R1} = I_{R2} R_2 + I_{R1} R_1 = I_{R1} (R_2 + R_1) + V_{C1}$$

$$= R_2 \frac{V_{C1}}{R_1} + R_1 C_1 \dot{V}_{C1} + V_{C1}$$

$$L_2 = C_2 \ddot{v}_{C_2} = C_2 \left(\frac{R_2}{R_1} \dot{v}_{C_1} + R_2 C_1 \ddot{v}_{C_1} + \dot{v}_{C_1} \right)$$

$$I_s = \frac{v_{C_1}}{R_1} + C_1 \dot{v}_{C_1} + \frac{C_2 R_2}{R_1} \dot{v}_{C_1} + C_1 C_2 R_2 \ddot{v}_{C_1} + C_2 \dot{v}_{C_1}$$

$$C_1 C_2 R_2 \ddot{v}_{C_1} + [C_1 + C_2 R_2 / R_1 + C_2] \dot{v}_{C_1} + \frac{1}{R_1} v_{C_1} = I_s$$

$$\ddot{v}_{C_1} + \left[\frac{1}{C_2 R_2} + \frac{1}{C_1 R_1} + \frac{1}{C_1 R_2} \right] \dot{v}_{C_1} + \frac{1}{C_1 C_2 R_2} v_{C_1} = \frac{I_s}{C_1 C_2 R_2}$$

$$b. i. p(s) = X_0 \left(\frac{1}{C_2 R_2} + \frac{1}{C_1 R_1} + \frac{1}{C_1 R_2} \right) X_0 + \frac{1}{C_1 C_2 R_2} = 0$$

$$\Rightarrow X^2 + \left(2H_2 + \frac{3}{2}H_2 + \frac{1}{2}H_2 \right) X + \frac{3}{1/2} = 0$$

$$\Rightarrow X^2 + 4H_2 X + 3/s^2 = 0$$

$$\Rightarrow X = -2H_2 \text{ or } X = -3/s^2 \quad \checkmark$$

$$i. v_{C_1}(t) = A_1 e^{-2t} + A_2 e^{-3t} \quad \checkmark$$

ii. By inspection from the equation,

$$v_{C_1}(t) = \frac{-I_s}{R_1} = \frac{-I_s}{1/2} \quad t > 0 \quad \checkmark$$

10. At $t=0^-$, both capacitors have zero voltage. By continuity, $v_{C_1}(0^+) = 0$. Similarly, since v_{C_2} is continuous, $v_{C_2}(0^+) = 0$. This means no current flows through R_1 or R_2 , so no current can flow through C_1 . $\frac{dv_{C_1}}{dt} \Big|_{t=0^+} = 0$

$$v_{C_1}(t) = I_s / R_1 + A_1 e^{-2t} + A_2 e^{-3t}$$

$$v_{C_1}(0) = 0 \Rightarrow A_1 + A_2 = -I_s / R_1$$

$$v_{C_1}'(0) \Rightarrow -2A_1 - 3A_2 = 0$$

$$\Rightarrow A_1 = 3/2 I_s / R_1, \quad A_2 = -1/2 I_s / R_1$$

$$v_{C_1}(t) = \frac{I_s}{1/2} + \frac{3I_s}{2/2} e^{-2t} - \frac{I_s}{2/2} e^{-3t}$$




3. A

3

Before time 0, there is no energy, voltage, or current. For $t > 0$, the inductor is short-circuited so no current flows through it. The current I_s is applied to the capacitor.
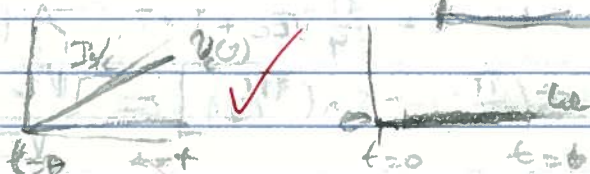
$$V_c = I_s t \Rightarrow \boxed{V_c(t) = \frac{I_s t}{C}, \quad I_L(t) = 0}$$



b. At this point, the circuit is an undriven LC circuit. The initial $V_c(T) = I_s T / C, I_L(T) = 0$


The differential equation for the circuit is $\frac{d^2 V_c(t)}{dt^2} + \frac{1}{LC} V_c(t) = 0$. It is solved

$$\text{by } \boxed{V_c(t) = \frac{I_s T}{C} \cos\left(\frac{t-T}{\sqrt{LC}}\right)}$$

$$\boxed{I_L(t) = -C \frac{dV_c}{dt} = \frac{I_s T}{\sqrt{LC}} \sin\left(\frac{t-T}{\sqrt{LC}}\right)}$$

When the cosine term is zero, the sine term is 1

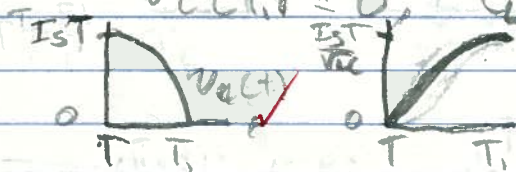
$$V_c(T_1) = 0, \quad I_L(T_1) = \frac{I_s T}{\sqrt{LC}}$$



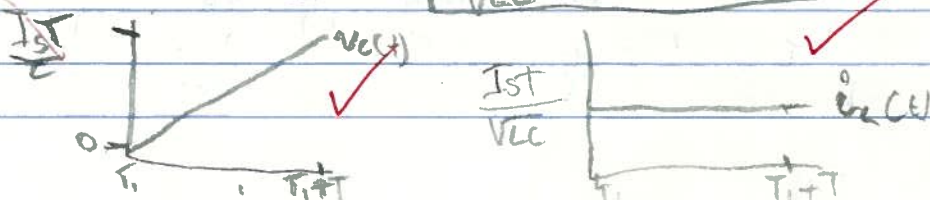c. The current through the inductor does not change, because the voltage across the inductor is zero. The current source charges the inductor exactly as in part a.

$$C \frac{dV_c}{dt} = I_s \Rightarrow \boxed{V_c(t) = \frac{I_s}{C} (t - T_1)}$$

$$\boxed{I_L(t) = I_L(T_1) = \frac{I_s T}{\sqrt{LC}}$$



d. This is an undriven LC circuit with sinusoidal response.




$$\frac{d^2 V_C}{dt^2} + \frac{1}{LC} V_C = 0 \quad \text{The initial conditions are } V_C(0) = 0$$

imply that $V_C(t) = \frac{I_s T}{C} \cos\left(\frac{t - (T_1 + T)}{\sqrt{LC}}\right) - \frac{I_s T}{C} \sin\left(\frac{t - (T_1 + T)}{\sqrt{LC}}\right)$

$$\Rightarrow L \dot{I}_C(t) = -e V_C = \frac{I_s T}{\sqrt{LC}} \cos\left(\frac{t - (T_1 + T)}{\sqrt{LC}}\right) + \frac{I_s T}{\sqrt{LC}} \sin\left(\frac{t - (T_1 + T)}{\sqrt{LC}}\right)$$

$V_C(t) = 0$ at $t = \frac{\pi}{\omega} \sqrt{LC} + T_1 + T$. At this time
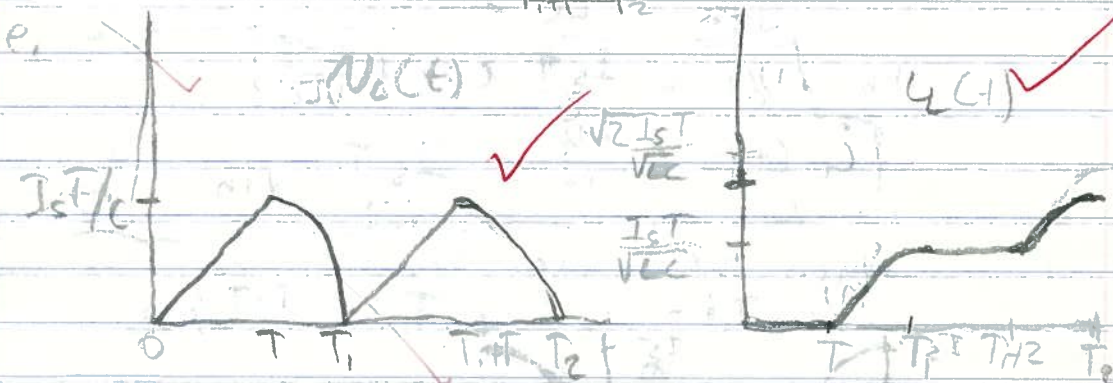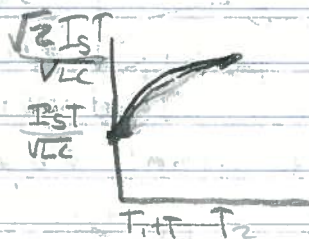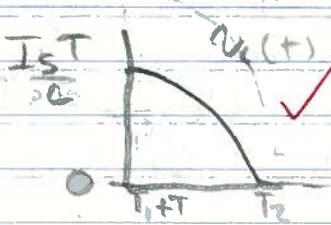
$$L \dot{I}_C(t_2) = \frac{I_s T}{\sqrt{LC}} [\cos(\frac{\pi}{2}) - \sin(\frac{\pi}{2})] = \frac{\sqrt{2} I_s T}{\sqrt{LC}}$$



2) 9.4. a $V_C(t) = I_s T / C$ from above
 \Rightarrow energy in cap = $\frac{1}{2} C V_0^2 = \frac{1}{2} I_s^2 T^2 / C$

b Energy in inductor = $\frac{1}{2} L I_0^2$. The energy
 $\frac{1}{2} I_s^2 T^2 / C = \frac{1}{2} L I_0^2 \Rightarrow I_0 = \frac{I_s T}{\sqrt{LC}}$

$$\Rightarrow I_C(T_1) = \frac{I_s T}{\sqrt{LC}}$$

c. The capacitor voltage at $t = T_1 + T$ is $I_s T / C$ from above.

$$E = \frac{1}{2} C V_C(T_1 + T)^2 = \frac{1}{2} \frac{I_s^2 T^2}{C}$$

d. The initial energy in the inductor is $\frac{1}{2} L i_L^2(T_1 + T)^2 = \frac{1}{2} L \frac{I_s^2 T^2}{LC} = \frac{1}{2} \frac{I_s^2 T^2}{C}$

The capacitor contains energy $\frac{1}{2} I_s^2 T^2 / C$ which is transferred to the inductor, giving it a final energy of $I_s^2 T^2 / C$

$$\frac{1}{2} L i_L^2(T_2)^2 = I_s^2 T^2 / C$$

$$i_L^2(T_2)^2 = \frac{2 I_s^2 T^2}{LC}$$

$$i_L(T_2) = \frac{\sqrt{2} I_s T}{\sqrt{LC}}, \text{ as expected.}$$

e. After n cycles, the energy on the inductor will be $n \cdot \frac{1}{2} I_s^2 T^2 / C$

$$\frac{1}{2} L i_L^2 = \frac{1}{2} n I_s^2 T^2 / C$$

$$\Rightarrow i_L^2 = \frac{n I_s^2 T^2}{LC}$$

$$\Rightarrow i_L = \frac{\sqrt{n} I_s T}{\sqrt{LC}}$$

1. The first part of the problem is to find the area of the region bounded by the curve $y = \sqrt{x}$ and the line $y = x$ from $x = 0$ to $x = 1$.

2. The second part is to find the volume of the solid generated by revolving the region about the y-axis.

3. The third part is to find the volume of the solid generated by revolving the region about the x-axis.

4. The fourth part is to find the volume of the solid generated by revolving the region about the line $x = 2$.

5. The fifth part is to find the volume of the solid generated by revolving the region about the line $x = 1$.

6. The sixth part is to find the volume of the solid generated by revolving the region about the line $x = 0$.

7. The seventh part is to find the volume of the solid generated by revolving the region about the line $x = 1$.

8. The eighth part is to find the volume of the solid generated by revolving the region about the line $x = 2$.

9. The ninth part is to find the volume of the solid generated by revolving the region about the line $x = 3$.

10. The tenth part is to find the volume of the solid generated by revolving the region about the line $x = 4$.

11. The eleventh part is to find the volume of the solid generated by revolving the region about the line $x = 5$.

12. The twelfth part is to find the volume of the solid generated by revolving the region about the line $x = 6$.