

Dan Ports
6.111 Lab 1
PAL SR Latch logic diagram

