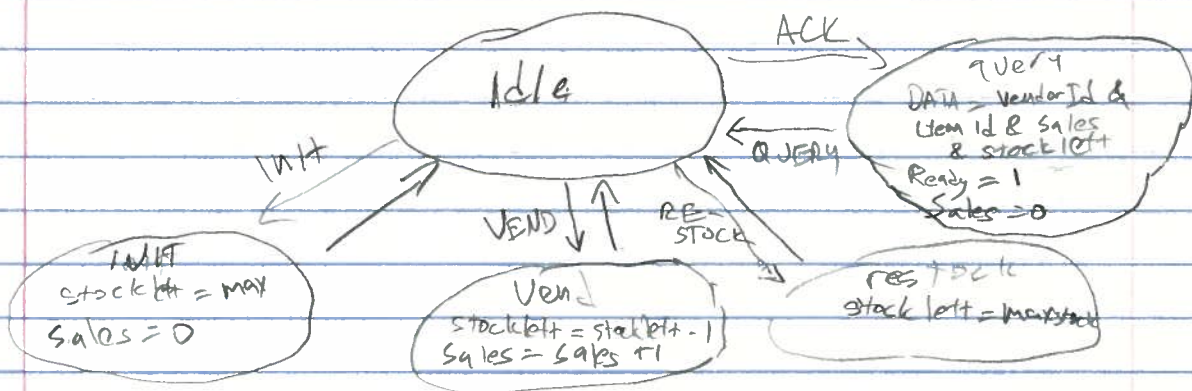


9/10

Simulation?


Dan Ports
6.11.15

I. Vendor FSM state diagram




II. See attached VHDL code.

III. Central controller state diagram

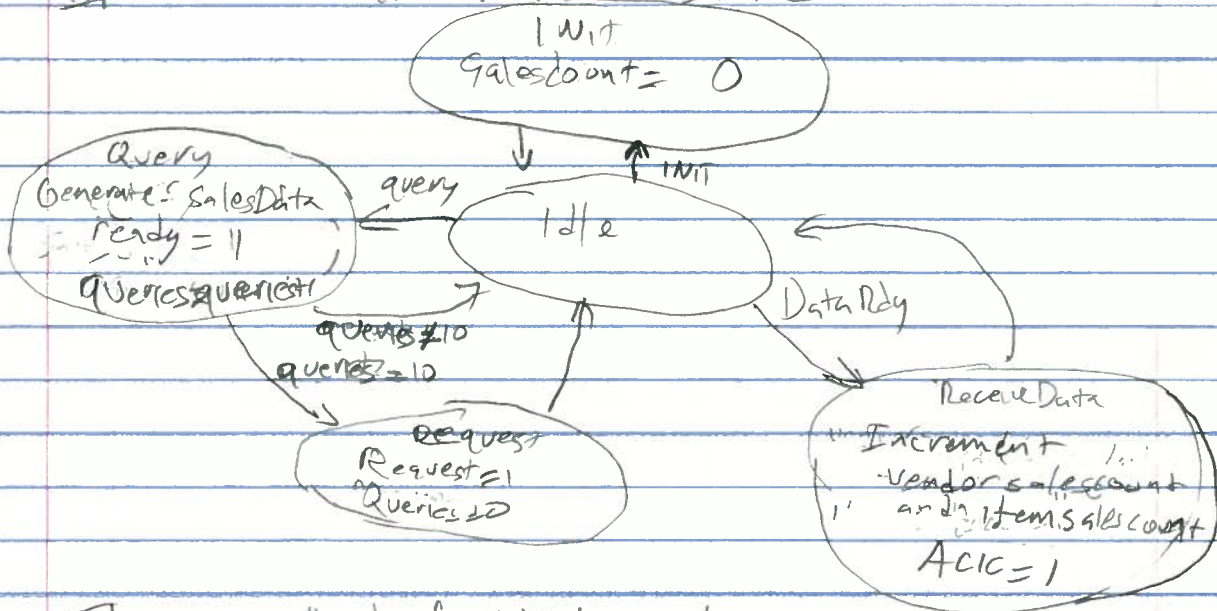

 IV. see attached VHDL code

Handwritten notes at the top of the page, including the word "metabolism" and some illegible scribbles.



```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use ieee.std_logic_arith.all;

entity vendor is

    generic (
        vendorid : integer := 0;
        itemid    : integer := 0);

    port (
        init, vend, restock, query, ack, clk : in  std_logic;
        ready                                : out std_logic;
        data                                  : out std_logic_vector(17 downto 0));

end vendor;

architecture behavioral of vendor is

    type StateType is (s_idle, s_init, s_vend, s_query, s_restock);
    signal p_s, n_s : StateType;
    signal vendoridvec : std_logic_vector(5 downto 0);
    signal itemidvec   : std_logic_vector(2 downto 0);
    signal sales       : std_logic_vector(4 downto 0);
    signal maxstock, stockleft : std_logic_vector(3 downto 0);

begin -- behavioral

    -- purpose: generate next state
    -- type    : combinational
    -- inputs  : p_s, init, vend, restock, query
    -- outputs : n_s
    nextstate: process (p_s, init, vend, restock, query)
    begin -- process nextstate
        if p_s = s_idle then
            if init = '1' then
                n_s <= s_init;
            elsif vend = '1' then
                n_s <= s_vend;
            elsif restock = '1' then
                n_s <= s_restock;
            elsif query = '1' then
                n_s <= s_query;
            else
                n_s <= s_idle;
            end if;
        elsif p_s = s_query then
            ready <= '1';
            if ack = '1' then
                n_s <= s_idle;
            else
                n_s <= s_query;
            end if;
        else
            n_s <= s_idle;
        end if;
    end process nextstate;

    -- purpose: perform state transitions on clock edge and generate output
    -- type    : combinational
    -- inputs  : clk
    -- outputs : p_s, n_s
    state_clocked: process (clk)
    begin -- process state_clocked
        if rising_edge(clk) then

```

```

p_s <= n_s;
if n_s = s_init then
  stockleft <= maxstock;
  sales <= (others => '0');
  vendoridvec <= conv_std_logic_vector(vendorid, 6);
  itemidvec <= conv_std_logic_vector(itemid, 3);
  case itemid is
    when 0 => maxstock <= "1100";
    when 1 => maxstock <= "1010";
    when 2 => maxstock <= "1000";
    when 3 => maxstock <= "1010";
    when 4 => maxstock <= "1100";
    when 5 => maxstock <= "1000";
    when others => null;
  end case;
elseif n_s = s_vend then
  sales <= sales + 1;
  stockleft <= stockleft - 1;
elseif n_s = s_restock then
  stockleft <= maxstock;
elseif n_s = s_query then
  data <= vendoridvec & itemidvec & sales & stockleft;
  sales <= (others => '0');
end if;
end if;
end process state_clocked;

```

```

end behavioral;

```

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;

entity centralcontrol is

  port (
    clk, init, query, datardy : in std_logic;
    qid                        : in std_logic_vector(7 downto 0);
    data                       : in std_logic_vector(17 downto 0);
    ack, ready, request       : out std_logic;
    salesdata                  : out std_logic_vector(15 downto 0));

end centralcontrol;

architecture behavioral of centralcontrol is

  type salestype is array(63 downto 0) of std_logic_vector(15 downto 0);
  signal vendorsalescount, itemsalescount : salestype;

  type statetype is (s_idle, s_init, s_query, s_receivedata, s_request);
  signal p_s, n_s : statetype;

  signal queries : std_logic_vector(3 downto 0);

begin -- behavioral

  -- purpose: generate next state
  -- type    : combinational
  -- inputs  : p_s, query, datardy, init
  -- outputs : n_s
  next_state: process (p_s, query, datardy, init)
  begin -- process next_state

    case p_s is
      when s_idle =>
        if init = '1' then
          n_s <= s_init;
        elsif query = '1' then
          n_s <= s_query;
        elsif datardy = '1' then
          n_s <= s_receivedata;
        else
          n_s <= s_idle;
        end if;
      when s_init => n_s <= s_idle;
      when s_query => if queries = 10 then
        n_s <= s_request;
      else
        n_s <= s_idle;
      end if;
      when s_request => n_s <= s_idle;
      when s_receivedata => n_s <= s_idle;
      when others => n_s <= s_idle;
    end case;

  end process next_state;

  -- purpose: perform state transitions and generate outputs
  -- type    : combinational
  -- inputs  : clk
  -- outputs : p_s, ready, salesdata, request, salescount, queries, ack
  state_clocked: process (clk)
  begin -- process state_clocked
    p_s <= n_s;
  end process state_clocked;
end architecture behavioral;

```

```

case n_s is
  when s_idle => ready <= '0'; request <= '0'; ack <= '0';
  when s_init => ready <= '0'; request <= '0'; ack <= '0';
  when s_request => ready <= '0'; request <= '1'; ack <= '0';
    queries <= (others => '0');
  when s_receivedata => ready <= '0'; request <= '0'; ack <= '1';
    vendorsalescount(conv_integer(data(17 downto 11))) <= ve
ndorsalescount(conv_integer(data(17 downto 11))) + 1;
    itemsalescount(conv_integer(data(10 downto 8))) <= items
alescount(conv_integer(data(10 downto 8))) + 1;
  when s_query => ready <= '1'; request <= '0'; ack <= '0';
    queries <= queries + 1;
    if qid(7) = '1' then
      salesdata <= itemsalescount(conv_integer(qid(5 downto 2)));
    else
      salesdata <= vendorsalescount(conv_integer(qid(5 downto 0)))
;
      end if;
    when others => null;
  end case;

end process state_clocked;

end behavioral;

```